

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V (Old) EXAMINATION – WINTER 2019

Subject Code: 150902

Date: 06/12/2019

Subject Name: Power System Analysis And Simulation

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:


1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Derive equivalent- π circuit of a long transmission line. 07
 (b) A three phase, 60 Hz transmission line, 130 Km long delivering 270 MVA at 325 kV & a 0.8 p.f. lagging. The resistance & inductance of the lines per phase per km are 0.036Ω & 0.8 mH respectively, While capacitance is $0.0112 \mu\text{F} / \text{km} / \text{phase}$. Using Nominal-T method. Calculate:
 (1) Sending end Voltage (2) Sending end Current (3) Voltage regulation and (4) Line efficiency. 07


- Q.2** (a) Write a brief note on selection of circuit breakers. 07
 (b) Explain in brief transients in RL series circuits 07

OR

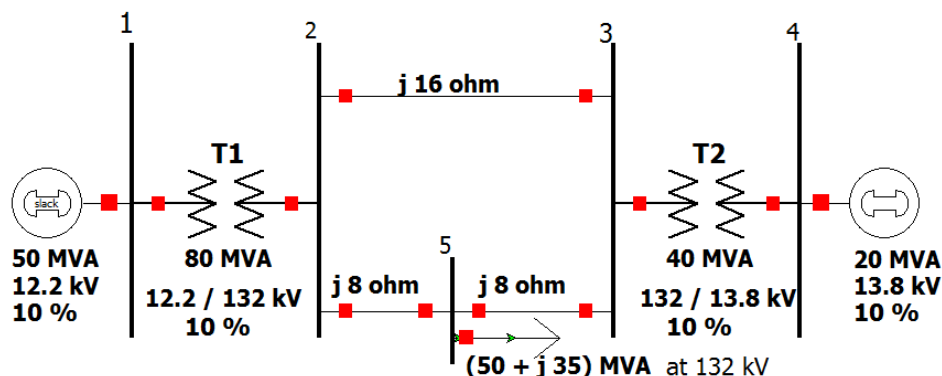- (b) Draw the reactance diagram & mark all reactance in per unit. Choose 12.2 kV as a base for generator & 50 MVA. 07




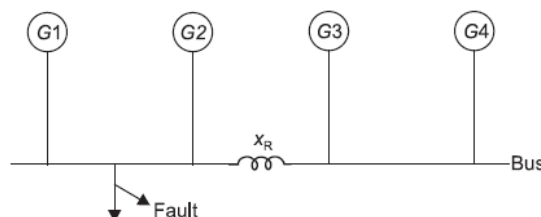- Q.3** (a) Derive the necessary equations to convert: (i) phase quantities into symmetrical components (ii) symmetrical components in to phase quantities. 07
 (b) Figure shows a system having four synchronous generators each rated 11.2 kV, 60 MVA and each having a subtransient reactance of 16%. Find (a) fault level for a fault on one of the feeders (near the bus with $X_R = 0$). (b) The reactance of the current limiting reactor X_R to limit the fault level to 860 MVA for a fault on one of the feeders near the bus. 07



OR

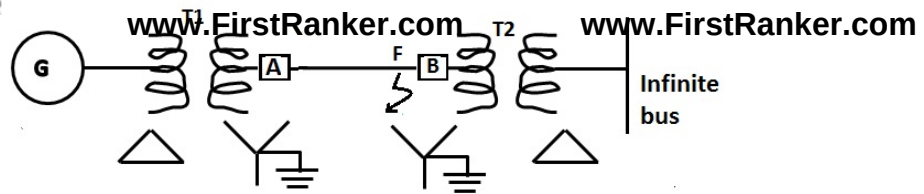- Q.3** (a) Prove that zero impedance of fully transposed transmission lines is always higher than positive and negative sequence impedances. 07
 (b) The System shown in Fig. is delivering 50 MVA at 11 kV, 0.8 lagging power factor into a bus which may be regarded as infinite. 07



Generator: 60 MVA, 12 kV, $X'_d = 35\%$
Transformer (each): 80 MVA, 12/66 kV, $X = 8\%$
Line: $X = 12 \Omega$

Calculate the symmetrical current that the circuit breaker A and B will be called upon to interrupt in the event of a three phase fault occurring at F near the circuit breaker B.

- Q.4 (a)** Explain line to ground fault on an unloaded generator using symmetrical components. **07**
- (b)** A 25 MVA, 11 kV generator has $X_1 = 0.2$ p.u., $X_2 = 0.3$ p.u. and $X_0 = 0.1$ p.u.. The neutral of the generator is solidly grounded. Determine the sub-transient current in the generator and the line-to-line voltages for sub-transient condition when a Y-B fault occurs at the generator terminals. Assume pre-fault currents and fault-resistance to be zero. **07**

OR

- Q.4 (a)** Derive an expression for fault current for double line-to-ground fault by symmetrical components method. **07**
- (b)** A three phase, 37.5 MVA, 33 kV alternator having $X_1 = 0.18$ pu, $X_2 = 0.12$ pu and $X_0 = 0.10$ pu, based on its ratings, is connected to a 33 kV overhead line having $X_1 = 6.3$ ohms, $X_2 = 6.3$ ohms and $X_0 = 12.6$ ohms per phase. A single line to ground fault occurs at the remote end of the line. The alternator neutral is solidly grounded. Calculate fault current. **07**
- Q.5 (a)** Explain the need of neutral grounding of system. Describe any one method of neutral grounding. **07**
- (b)** A grid line operating at 132 kV consists of 2 cm diameter conductors spaced 4 meters apart. Determine the disruptive critical voltage and visual corona voltage for the following data: Temperature 44°C , barometric Pressure 73.7 cm of mercury, conductor surface factor 0.84, fine weather 0.8 and rough weather 0.66. **07**

OR

- Q.5 (a)** Briefly discuss the factors affecting Corona. **07**
- (b)** Explain the phenomena of arcing grounds. How does neutral grounding eliminate the arcing ground? **07**
