

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER- III (New) EXAMINATION – WINTER 2019****Subject Code: 2130305****Date: 3/12/2019****Subject Name: Analog Circuits-I****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

**MARKS**

- Q.1** (a) Define biasing and state the need for biasing. **03**  
 (b) Draw and explain half wave and full wave rectifier. **04**  
 (c) Draw and explain output characteristics of CE configuration. **07**
- Q.2** (a) State different configurations of BJT. Define  $\alpha$  and  $\beta$  of a transistor. **03**  
 (b) Compare JFET with BJT **04**  
 (c) Explain the operation of JFET and derive the drain and transfer characteristics. **07**
- OR**
- (c) With neat diagram explain the operation of MOSFET in Enhancement mode and derive its current equations **07**
- Q.3** (a) The transistor has  $I_E = 10 \text{ mA}$  and  $\alpha = 0.98$ . Find the value of base and collector currents. **03**  
 (b) Draw the V-I characteristics curve of MOSFET. Explain each parameter. **04**  
 (c) Draw and explain the various types of negative feedback connection. **07**
- OR**
- Q.3** (a) Give the pin-diagram of IC 741 and illustrate the concept of virtual ground. List out the ideal characteristics of Op-amp. **03**  
 (b) Define: 1) Input offset Voltage 2) Input offset Current 3) Slew Rate 4) CMRR **04**  
 (c) Draw the circuit diagram of op-amp Integrator and derive an expression for the output in terms of the input. **07**
- Q.4** (a) What is the need for an instrumentation amplifier? List the features of the instrumentation amplifier. **03**  
 (b) Draw the subtractor circuit using op-amp and mention its applications. **04**  
 (c) With neat diagram explain Sample and hold circuit. **07**
- OR**
- Q.4** (a) Explain the voltage to current converter. **03**  
 (b) With the help of a block diagram, explain the various stages present in an operational amplifier **04**  
 (c) Design Phase shift Oscillator so that  $F_0 = 200 \text{ Hz}$ . **07**
- Q.5** (a) Give any four application of Comparator. **03**  
 (b) Explain the working of Log amplifier with the help diagram. **04**  
 (c) Design Wein Bridge Oscillator so that  $F_0 = 965 \text{ Hz}$ . **07**
- OR**
- Q.5** (a) What is the difference between normal rectifier and precision rectifier? **03**  
 (b) Draw and explain the circuit diagram of a peak detector. **04**  
 (c) Draw and explain the circuit diagram for Inverting comparator as Schmitt trigger for  $R_1 = 100\Omega$ ,  $R_2 = 56\text{k}\Omega$ ,  $V_{in} = 1\text{Vpp}$  Sinewave. Determine the threshold voltage and draw the output waveform. **07**

\*\*\*\*\*