

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– VI (New) EXAMINATION – WINTER 2019****Subject Code: 2162003****Date: 04/12/2019****Subject Name: Control of Electric Drives****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

|  | Marks     |
|--|-----------|
| <b>Q.1</b> (a) What is power modulator? List out.  | <b>03</b> |
| (b) What is electric drive? Draw block diagram.  | <b>04</b> |
| (c) Describe the choice of electric drives.  | <b>07</b> |
| <b>Q.2</b> (a) What is steady state stability?   | <b>03</b> |
| (b) Derive fundamental torque equation for drive.  | <b>04</b> |
| (c) Derive the mathematical model of separately excited DC machine.                                  | <b>07</b> |
| <b>OR</b>  |           |
| (c) Explain the four quadrant operation of electrical drive with example.                            | <b>07</b> |
| <b>Q.3</b> (a) Explain how to determine the moment of inertia of drive system.                       | <b>03</b> |
| (b) In snubber circuit why we use the resistor?  | <b>04</b> |
| (c) Explain various PWM techniques for single phase inverter and three phase inverter.               | <b>07</b> |
| <b>OR</b>  |           |
| <b>Q.3</b> (a) List out turn on methods of thyristor.  | <b>03</b> |
| (b) Describe single phase inverter in brief.   | <b>04</b> |
| (c) Explain in brief various control strategies of a chopper.  | <b>07</b> |
| <b>Q.4</b> (a) Define the terms: (1) latching current (2) holding current (3) circuit turn-off time. | <b>03</b> |
| (b) Explain the principle of phase control rectifiers.   | <b>04</b> |
| (c) Explain the series operation of thyristor.   | <b>07</b> |
| <b>OR</b>  |           |
| <b>Q.4</b> (a) Give the classification of Choppers.  | <b>03</b> |
| (b) How voltage control in single phase bridge inverter.   | <b>04</b> |
| (c) Explain A.C. phase control of TRIAC using DIAC.  | <b>07</b> |
| <b>Q.5</b> (a) Enlist methods of braking in DC motors.   | <b>03</b> |
| (b) Explain transient analysis in DC motor drives.   | <b>04</b> |
| (c) Give the comparison between various methods of braking in dc motors.                             | <b>07</b> |
| <b>OR</b>  |           |
| <b>Q.5</b> (a) Explain any one speed control method of 3-phase induction motor in detail.            | <b>03</b> |
| (b) Explain with necessary diagram 3-point starter using in dc motor.                                | <b>04</b> |
| (c) Explain the speed control method of 3-phase induction motor.                                     | <b>07</b> |