

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– VII (New) EXAMINATION – WINTER 2019****Subject Code: 2170808****Date: 28/11/2019****Subject Name: Sensor Networks & Instrumentation****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain V-I converters using OP-AMP. **03**
(b) What is Negative Feedback? What are its advantages? **04**
(c) What is Sensor? Give classification of sensors with respect to various parameters. **07**

- Q.2** (a) Explain KRC filters. **03**
(b) Explain Humidity sensors in details. **04**
(c) Explain first order low pass filter and derive all equations with neat figure **07**

OR

- (c) Explain Second Order Band Pass Filter in detail **07**
Q.3 (a) Explain Multiple Feedback filters. **03**
(b) Explain Capacitive sensor. **04**
(c) How to select a Sensor? Explain selection of sensor in detail. **07**

OR

- Q.3** (a) Explain Temperature Sensor in detail **03**
(b) Explain I to V converter. **04**
(c) Explain with neat sketch CO₂ Sensing techniques with necessary equations and graphs. **07**

- Q.4** (a) Explain characteristics of an Ideal OP-AMP. **03**
(b) Explain Zigbee Network. **04**
(c) Explain general architecture of smart sensor. **07**

OR

- Q.4** (a) Explain Block Diagram of OP-AMP. **03**
(b) What is the application area of Smart Sensors? **04**
(c) Explain various factors influencing WSN design. **07**

- Q.5** (a) What is wireless sensor network?. **03**
(b) Explain loading effect on sensors output **04**
(c) Explain First Order RC filters and derive its equations **07**

OR

- Q.5** (a) Explain Cascade design for Active Filters. **03**
(b) Derive equations for KRC filters. **04**
(c) Explain Transducer Bridge Amplifier using Op-Amp with Application. **07**
