

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER– III (New) EXAMINATION – WINTER 2019

Subject Code: 2130901

Date: 28/11/2019

Subject Name: Circuits and Networks

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) In terms of two terminal elements, define: 1) Unilateral elements, 2) Passive elements, 3) Time-variant elements. **03**
- (b) Draw circuit representations of ideal and practical voltage and current sources. How internal impedance affects the performance of practical voltage and current sources? **04**
- (c) For the network shown in figure 1, obtain the power loss in 4Ω and 5Ω resistors using mesh analysis. **07**

- Q.2** (a) Using equivalent circuit representations at $t=0+$, explain initial conditions in R, L and C elements. **03**
- (b) For the network shown in figure 1, obtain the power loss in 10Ω resistor using nodal analysis. **04**
- (c) Find out Z-parameters for the network of figure 2 **07**

OR

- (c) Find out ABCD parameters for the network of figure 3. **07**
- Q.3** (a) State and explain substitution theorem. **03**
- (b) For the network shown in figure 4, switch K is closed at $t=0$. The current waveform is observed with CRO. The initial value of the current is measured to be 0.01 A. The transient appears to disappear in 0.1 sec. Find: 1) The value of R, 2) The value of C, 3) The equation of $i(t)$. **04**
- (c) For the network given in figure 5, obtain equivalent circuit and hence find current in the branch AB using Thevenin's theorem. **07**

OR

- Q.3** (a) Give various properties of positive real functions. **03**
- (b) State and explain compensation theorem. **04**
- (c) In the network of figure 6, capacitor C_1 is charged to voltage V_0 and the switch is closed at $t=0$. When $R_1=2M\Omega$, $V_0=1000V$, $R_2=1M\Omega$, $C_1=10\mu F$ and $C_2=20\mu F$, solve for $\frac{d^2 i_2}{dt^2}$ at $t=0+$. **07**

- Q.4** (a) Draw general nature of time response of a system when: 1) Poles are complex conjugate having negative real part. 2) Poles are imaginary with zero real part. Give your comment on the two responses. **03**
- (b) Explain the properties of Hurwitz polynomial. **04**
- (c) RL series circuit with $R=25\Omega$ and $L=5H$ is connected to $V=100V$ dc supply at time $t=0$. With no initial current in inductor, find: 1) Equation for circuit current $i(t)$ 2) equations for voltage across R and L 3) Current in circuit at $t=0.5\text{sec}$ 4) Time 't' at which voltages across R and L become same. **07**

OR

- Q.4** (a) What are poles and zeroes of network functions? Explain their physical significance. **03**

- (b) State the advantages of network analysis using Laplace transformation. List out steps of obtaining solution of differential equation using Laplace transformation. 04
- (c) For a second order circuit, explain solution of non-homogeneous differential equations, clearly indicating all steps involved. Describe in detail, how particular integral can be evaluated using method of undetermined coefficients. 07
- Q.5** (a) Describe in brief, how solution of second order homogeneous differential equations can be obtained. 03
- (b) For the network shown in figure 7, without changing the node numbers, branch numbers and direction of branches shown in figure, obtain the reduced incidence matrix considering node 5 as the reference node. 04
- (c) In the circuit of figure 8, switch is moved to position 2 after being in position 1 for a very long time. Using Laplace transformation, obtain expression for $i(t)$ for $t > 0$. 07

OR

- Q.5** (a) Find the driving-point impedance for the network shown in figure 9. Arrange the polynomials with the highest-ordered term normalized to unity coefficient. 03
- (b) Draw the oriented graph from the reduced incidence matrix of the graph given as: 04
- $$A = \begin{bmatrix} 0 & 1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$
- (c) For the network shown in figure 7, without changing the node numbers, branch numbers and direction of branches shown in figure, obtain the tie-set and fundamental cut-set matrices considering the tree formed with branches 1, 2, 3 and 4 as the twigs of the tree. 07

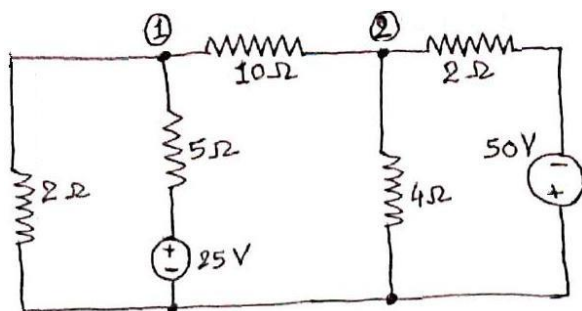


Figure 1

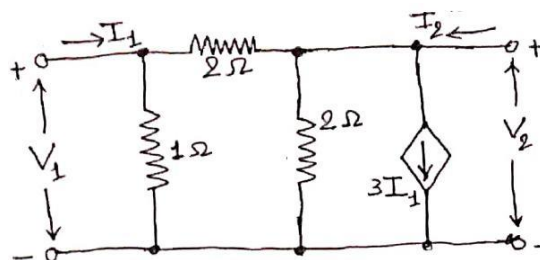


Figure 2

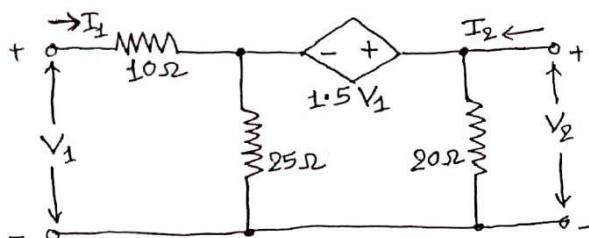


Figure 3

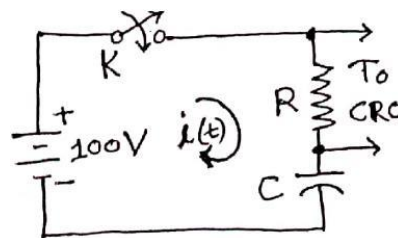


Figure 4

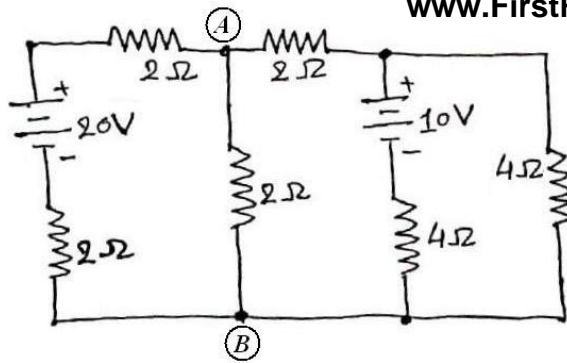


Figure 5

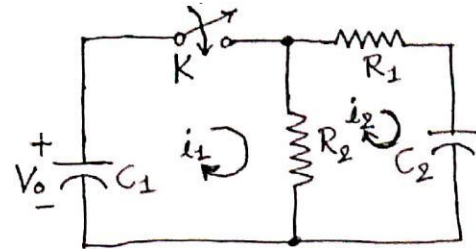


Figure 6

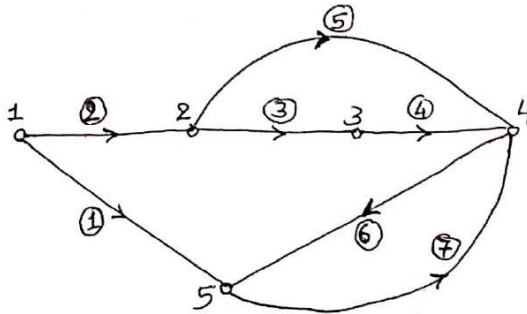


Figure 7

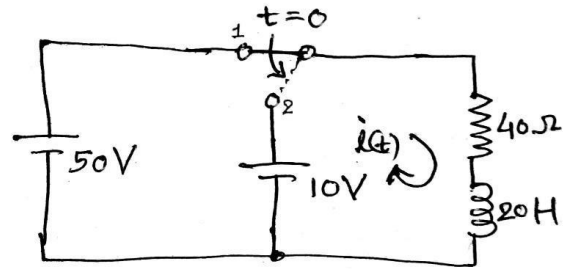


Figure 8

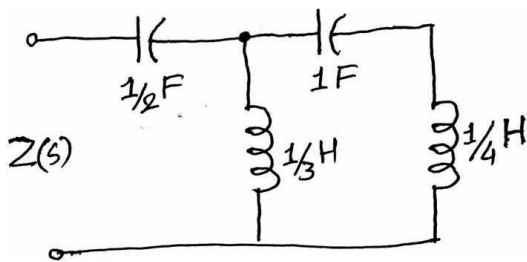


Figure 9

www.FirstRanker.com