

Seat No.: _____

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– VII (New) EXAMINATION – WINTER 2019****Subject Code: 2171707****Date: 23/11/2019****Subject Name: Industrial Drives and Control****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Why PWM inverter used to control speed of Induction motor? Explain in brief. **03**
(b) Explain various drive circuits for the stepper motors, in brief. **04**
(c) Discuss the basic working theory of DC servo motor. Find its governing equation and transfer function also. Derive state space modeling of DC motor drive with block diagram. **07**

- Q.2** (a) Why is the duty cycle usually changed by varying the on time rather than the chopping frequency? Explain in brief. **03**
(b) Discuss brushless DC motor and its speed control strategy. **04**
(c) Draw the waveforms of 1st Quadrant chopper operation for DC motor drive & Explain with relevant calculation. **07**

OR

- (c) Draw the waveforms of 3rd Quadrant chopper operation for DC motor drive & Explain with relevant calculation. **07**

- Q.3** (a) Explain torque versus stepping rate characteristics for Stepper motor. **03**
(b) Discuss the Merits and Demerits of Volts/ Hz control strategy for AC drive . **04**
(c) Explain Chopper principle used in electrical drive with circuit, waveform and equation. **07**

OR

- Q.3** (a) List out important features of the stepper motors. **03**
(b) Discuss the static frequency changers for AC motor drive, in brief. **04**
(c) Compare the performance features of six step and PWM control of Voltage-source inverter in terms of Harmonics, control complexity and ease of implementation. **07**

- Q.4** (a) State essential parts of Electrical drives. **03**
(b) What are factors that limit the high frequency operation of DC chopper switching operation? **04**
(c) Explain the operation of a Variable Reluctance stepper motor. **07**

OR

- Q.4** (a) What are the main factors which decide the choice of electrical drive for a given application? **03**
- (b) Discuss the various measuring scheme for motor constants with diagram/calculation for DC motor, in brief. **04**
- (c) Design a Digital controller for a hysteresis current control for DC chopper drive. **07**

- Q.5** (a) What are the functions of Power modulator? **03**
- (b) Explain multi-pulse modulation technique for the induction motor, in brief. **04**
- (c) What do you mean by DC servo motor closed loop speed control ? Explain it with diagram. **07**

OR

- Q.5** (a) Explain operation of Permanent Magnet stepper motor, in brief. **03**
- (b) Discuss in brief, Phase Locked Loop (PLL) control of the DC motor drive with block diagram. **04**
- (c) Explain the operation of half-bridge modified McMurray inverter. **07**

www.FirstRanker.com