

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER– III (New) EXAMINATION – WINTER 2019

Subject Code: 2131006

Date: 30/11/2019

Subject Name: Electronic Devices and Circuits

Time: 02:30 PM TO 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

MARKS


- Q.1** (a) Explain the second approximation of diode VI characteristics and equivalent circuit. **03**
- (b) How the depletion layer is formed in unbiased diode? **04**
- (c) Draw the circuit of Bridge rectifier and explain the operation of circuit for positive and negative half cycle of input signal. **07**

- Q.2** (a) What is the difference between rectifier diode and small signal diode? **03**
- (b) Write a short note on Varactor diode. **04**
- (c) For a negative biased clipper circuit, input voltage is 5V peak to peak sine wave with frequency of 1KHz. Biased voltage is set at 1.1V. Draw the circuit and input – output waveform for second approximation of germanium diode. **07**

OR

- (c) For a positive biased clipper circuit, input voltage is 6V peak to peak sine wave with frequency of 1KHz. Biased voltage is set at 0.9V. Draw the circuit and input – output waveform for second approximation of silicon diode. **07**

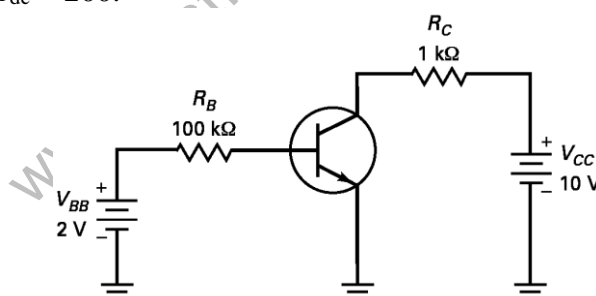
- Q.3** (a) Explain the T Model of a transistor. **03**
- (b) Use the second approximation to calculate the base current in below circuit. What is the voltage across the base resistor? Find the collector current if $\beta_{dc} = 200$. **04**



- (c) Explain the voltage divider bias circuit in detail. **07**

OR

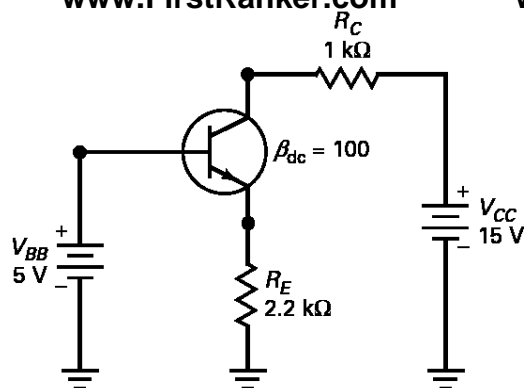- Q.3** (a) Draw the circuit of emitter follower and find its AC emitter resistance. **03**
- (b) For voltage divider bias CE amplifier, find the equation of voltage gain using π Model. **04**



- Q.4** (a) Explain Darlington pair connections of two transistors. **03**
 (b) Explain the difference of class A and class B operation of an amplifier. **04**
 (c) Draw the circuit of class B push – pull amplifier and explain its working. List the advantages and disadvantages. **07**

OR

- Q.4** (a) Draw the symbol of JFET, depletion MOSFET and enhancement MOSFET. **03**
 (b) Explain the common source amplifier using JFET. **04**
 (c) What is the frequency response of an amplifier? Explain the decibel power gain and decibel voltage gain with examples. **07**

- Q.5** (a) Why JFET is called as voltage controlled device? **03**
 (b) Explain the four types of negative feedback connections. **04**
 (c) Explain the structure and biasing arrangements of Enhancement Mode MOSFET for obtaining $I_D - V_{DS}$ curve. **07**

OR

- Q.5** (a) Explain the transconductance curve for JFET. **03**
 (b) What is the role of bypass capacitor in voltage divider bias amplifier? **04**
 (c) Explain the self bias technique for JFET. **07**
