

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER– III (New) EXAMINATION – WINTER 2019

Subject Code: 2132003
Date: 30/11/2019
Subject Name: Design Concepts in Basic Electronics
Time: 02:30 PM TO 05:00 PM
Total Marks: 70
Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Perform binary division of $(1100)_2$ and $(100)_2$ and find quotient, remainder and answer. **03**
- (b) Explain positive clamper and negative clamper with circuit diagrams. **04**
- (c) Explain the advantages of Digital System over Analog System. **07**
- Q.2** (a) Explain block diagram of digital system with its functional elements. **03**
- (b) Construct discrete circuit for NOR Gate using TTL. **04**
- (c) Explain NAND Gate as universal Gate. **07**

OR

- (c) Explain Common Emitter (CE) Configuration with its input and output characteristics. **07**
- Q.3** (a) What are intrinsic and extrinsic semiconductor materials? **03**
- (b) Explain circuit diagram and output waveforms of biased positive clipper. **04**
- (c) Simplify the following Boolean Expression. Validate using truth table. Also implement the circuit for minimized function using logic gates. **07**

$$(\bar{A} + \bar{A} + B)(\bar{B} + \bar{B} + C)$$

OR

- Q.3** (a) Explain the capacitor input filter with half wave rectifier. **03**
- (b) Construct two bit full adder combinational circuit. **04**
- (c) Simplify the following function using K-Map method. Also implement the circuit for minimized function using logic gates. **07**

$$F(A, B, C, D) = \Pi\{0, 1, 3, 4, 5, 7, 8, 9, 11, 12, 14, 15\}$$

- Q.4** (a) Perform BCD addition of $(1001)_2$ and $(0100)_2$. **03**
- (b) Explain 8×1 Multiplexer with circuit diagram. **04**
- (c) Explain the voltage Doubler, Tripler and Quadrupler circuits in details. **07**

OR

- Q.4** (a) Express $(-23)_{10}$ as 8-bit sign number using sign magnitude, 1's compliment and 2's compliment methods. **03**
- (b) Convert $(359)_{10}$ to octal number using repeated division by 8 method. **04**
- (c) Explain Voltage-Divider Bias Configuration with its advantage. **07**
- Q.5** (a) Explain full wave rectifier with wave forms. **03**
- (b) Explain J-K flip-flop with example and wave forms. **04**
- (c) Explain working of Serial-in to Serial-out (SISO) shift registers. **07**

OR

- Q.5** (a) Explain full wave bridge rectifier with wave forms. **03**
- (b) Construct and explain working of 3-bit decoder. **04**
- (c) Explain the Ideal, Second and Third approximation for diode in detail with example. **07**
