

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-IV(NEW) – EXAMINATION – SUMMER 2019****Subject Code:2140910****Date:13/05/2019****Subject Name: Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
1. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Find the XS-3 code of following decimal numbers (i) 26 (ii) 42 (iii) 63	03
	(b) Differentiate between combinational logic circuit and sequential logic circuit.	04
	(c) Explain why NAND and NOR are known as universal gates and construct AND, OR and NOT using the universal gates.	07
Q.2	(a) Convert the following Binary to Gray Code (i)1001 (ii)1010 (iii) 1011	03
	(b) Convert the following (i) $(4CD)_{16} = ()_2$ (ii) $(26.24)_8 = ()_{10}$	04
	(c) Simplify $Y = A'BCD' + BCD' + BC'D' + BC'D$ and implement using NAND gate only.	07
OR		
	(c) State and explain De Morgan's theorems with truth tables.	07
Q.3	(a) Explain minterm and maxterm.	03
	(b) Add 27.125 to -79.625 using 12-bit 2's complement arithmetic.	04
	(c) Minimize using K-map $f(A,B,C,D) = \Sigma(1,3,4,6,8,11,15)$ +d(0,5,7) also draw MSI circuit for the output.	07
OR		
Q.3	(a) Explain parity checking method of error detection.	03
	(b) Perform the decimal subtraction 206.7-147.8 in 8421 BCD code.	04
	(c) Discuss 4 – bit magnitude comparator in detail.	07
Q.4	(a) Explain full adder.	03
	(b) Explain R-2R ladder DAC with necessary diagram.	04
	(c) Draw 4 bit down counter, explain its working with timing diagram and truth table.	07
OR		
Q.4	(a) Discuss multiplexer with suitable diagram.	03
	(b) Explain terms Accuracy and settling time for DAC.	04
	(c) Describe 3 to 8 line decoder with logic diagram and truth table.	07
Q.5	(a) Compare SRAM with DRAM.	03
	(b) Draw the two input TTL NAND gate circuit with totem pole output.	04
	(c) Describe operation of D/A converter with binary – weighted resistors.	07
OR		
Q.5	(a) Compare SOP and POS.	03
	(b) Give comparison between EPROM and FLASH memory.	04
	(c) Describe the working of look-ahead-carry adder.	07
