

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– V(OLD) EXAMINATION – SUMMER 2019****Subject Code:151006****Date:10/06/2019****Subject Name:Applied Electronics****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain block diagram of IC 555. **07**
(b) Explain principle of LVDT and its operation. Also enlist its advantages and disadvantages. **07**

- Q.2** (a) What is regulated power supply? Draw and explain block diagram of SMPS. Also write advantage of SMPS. **07**
(b) What is universal Gate? Explain NOR and NAND gate as a universal Gate. **07**

OR

- (b) Find out the Boolean expression of the Full Adder sum and carry. Using by same expression give realization of Full adder circuits. **07**

- Q.3** (a) Draw the block diagram of an OP-AMP and explain the function of each block. **07**
(b) With the help of the block diagram, explain the operation of a single trace Cathode Ray Oscilloscope. **07**

OR

- Q.3** (a) Explain construction and principle of operation of photoconductive cell. **07**
(b) Write a short note on strain gauge transducers. **07**

- Q.4** (a) Draw the equivalent circuit of UJT and plot its characteristics. **07**
(b) Discuss any one closed – Loop op-amp configurations in detail. **07**

OR

- Q.4** (a) Explain construction and working of SCR using two transistor model. **07**
(b) Explain the principal and working of Thermocouple. Compare it with RTD. **07**

- Q.5** (a) What is Ideal Voltage source? Also explain factors affecting the voltage regulation with block diagram of Shunt voltage regulator. **07**
(b) Explain Liquid Crystal Display with necessary figures. **07**

OR

- Q.5** (a) Write a short note on Digital Multimeter. **07**
(b) What is Washing Machine? Properly explain the concept of fuzzy logic used in washing machine. **07**
