

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI(NEW) – EXAMINATION – SUMMER 2019****Subject Code:2162409****Date:16/05/2019****Subject Name:Power Electronic Circuits – II****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What is significance of THD ? Give its equation. **03**
(b) Describe single phase bridge inverter with R load with gate and output waveforms. **04**
(c) Describe different methods for inverter output control. **07**
- Q.2** (a) Define harmonic factor. **03**
(b) Explain the principle of operation of resonant converters. **04**
(c) Write a short note on three phase inverter with 120° conduction mode **07**
- OR**
- (c) Draw single phase bridge inverter with RL load. Also draw its load voltage and load current waveforms. **07**
- Q.3** (a) Define odd and even symmetry of waveform with example. **03**
(b) Define quarter wave symmetry and discuss its significance in Fourier analysis of waveform. **04**
(c) Derive THD of square wave output wave form of an inverter. **07**
- OR**
- Q.3** (a) Sketch unipolar and bipolar modulated inverter output voltage waveform. **03**
(b) Explain advantages of active front end rectifier. **04**
(c) Explain integral cycle control and derive equation for its output voltage. **07**
- Q.4** (a) Explain cascaded H-bridge multilevel inverter in brief. **03**
(b) Why dead band is required in inverter gating pulses ? **04**
(c) Write a short note on SVPWM. **07**
- OR**
- Q.4** (a) Give comparison of voltage source and current source inverters. **03**
(b) Explain techniques for generating dead band for inverter switches. **04**
(c) Explain 3 level diode clamped multilevel inverter (DCMLI) with necessary diagrams. **07**
- Q.5** (a) Why various PWM techniques are required in inverter ? **03**
(b) Explain sine PWM technique with diagram. **04**
(c) Explain L-type ZCS resonant converter with circuit diagram and waveforms. **07**
- OR**
- Q.5** (a) Give classification of multilevel inverter. **03**
(b) Give merits of multilevel inverter technology. **04**
(c) Explain the McMurray-Bedford half-bridge inverter with circuit diagram and Waveforms. **07**
