

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2019****Subject Code: 2130306****Date: 18/06/2019****Subject Name: Fundamentals of Digital Design****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Perform BCD subtraction using 9's complement for : (151.6 - 89.7) ₁₀	03
	(b) Draw logic symbols for Bubbled-AND & NOR gate. Prove that both give same output using truth table.	04
	(c) Draw AOI logic for (A'B + AB') and convert it to NAND and NOR logic.	07
Q.2	(a) Which are called Universal Logic Gates? Explain with one example why?	03
	(b) Expand A(B' + A)B to maxterms and minterms.	04
	(c) Reduce the following expression using K-map and implement it in universal logic: $\Sigma m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$	07
	OR	
	(c) Minimize the following expression using tabulation method: $\Sigma m(0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$	07
Q.3	(a) Explain Half-subtractor in detail with equations and NOR logic circuit.	03
	(b) Explain 4x1 multiplexer in detail.	04
	(c) Design 2-bit parallel adder using Look-Ahead Carry.	07
	OR	
Q.3	(a) Explain Half-adder in detail with equations and NAND logic circuit.	03
	(b) Explain 4-bit ripple adder with block diagram.	04
	(c) Design a combination circuit where input given at D ₁ of 2x1 multiplexer can be displayed at D ₃ output of 1x4 demultiplexer.	07
Q.4	(a) What are Active-High and Active-Low configurations? Explain in detail.	03
	(b) Explain edge triggered D Flip flop.	04
	(c) Explain NAND gate S-R latch and NOR Gate S-R latch with truth table and Logic circuit.	07
	OR	
Q.4	(a) List different applications of Flip-Flops.	03
	(b) Explain edge triggered T Flip flop.	04
	(c) Explain edge triggered JK Flip-flop for Active-High and Active-Low configuration.	07
Q.5	(a) For DAC define: (1) Resolution, (2) Settling time (3) Offset Voltage	03
	(b) Explain Programmable Array Logic (PAL) with basic circuit structure.	04
	(c) Explain Serial-IN Serial-OUT shift register.	07

- Q.5**
- (a)** List types of A/D convertors. **03**
 - (b)** Using simplified connection method in PLA circuits draw circuit for following functions: **04**
 $F_1 = AB'C + A'B'C + AC$
 $F_2 = ABC + AB' + C$
 - (c)** Explain BCD to Seven Segment decoder for common-cathode LED display. **07**

www.FirstRanker.com