

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2019

| Subject Code: 2130904 | Date: 18/06/2019 |
|-----------------------|------------------|
| | |

Subject Name: DC Machines and Transformer

| Time: 02:30 PM TO 05:00 PM Total | al Marks: 70 |) |
|----------------------------------|--------------|---|
|----------------------------------|--------------|---|

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.

| | 3. Figures to the right indicate full marks. | | MADIZO |
|-----|--|--|--------|
| | | | MARKS |
| Q.1 | (a) | What are different parts of a DC machine? Explain the use of commutator. | 03 |
| | (b) | (b) Explain construction and working principle of auto-transformer. | |
| | (c) | Define armature reaction. Explain armature reaction effect in DC machine. How it can be minimized? | 07 |
| Q.2 | (a) | Mention the conditions for satisfactory parallel operation of three phase transformers. | 03 |
| | (b) | Explain the internal and external characteristics of D.C. Shunt Generator. | 04 |
| | (c) | The armature of a 230-volt shunt motor has a resistance of 0.18 ohm. If the armature current is not to exceed 76 amp, calculate: (a) the resistance that must be inserted in series with the armature at the instant of starting; (b) the value to which this resistance can be reduced when the armature accelerates until Ec is 168 volts; (c) the armature current at the instant of starting if no resistance is inserted in the armature circuit. (Assume a 2-volt drop at the brushes.). | 07 |
| | (c) | Explain voltage build up process of D.C. Generator. Also derive E.M.F. equation of D.C. Generator. | 07 |
| Q.3 | (a) | Why transformer rating is in KVA? | 03 |
| | (b) | Write a short note on current transformer and its applications. | 04 |
| | (c) | Terminal voltage of a long-shunt compound generator is 230 V when it delivers 150 A. Determine (i)Induced emf (ii) total power generated by armature. Consider: Shunt field resistance = 92 Ω , Series field = 0.015 Ω , Series field diverter resistance = 0.032 Ω . | 07 |
| Q.3 | (a) | Explain Scott connection of 3-phase transformer. | 03 |
| ₹ | (b) | Explain: compensating winding and interpoles in dc machine. | 04 |
| | (c) | Discuss essential and desirable conditions to be satisfied for parallel operation of two single phase transformers. | 07 |
| Q.4 | (a) | Draw and differentiate between long shunt & short shunt compound generator. | 03 |
| | (b) | Explain the load characteristics of DC shunt generator. | 04 |

07

(c) What is the necessity of starter in DC motor? Explain three point

starter with neat sketch.



| | | www.FirstRaffker.com www.FirstRank | |
|-----|------------|---|-----------|
| Q.4 | (a) | Explain "All day efficiency" of the transformer. | 03 |
| | (b) | Explain critical field resistance of d.c. shunt generator with its | 04 |
| | | significance | |
| | (c) | A 20 kVA, 2200/220 V, 50 Hz, 1- phase transformer gave the | 07 |
| | | following readings. | |
| | | O.C test: 220 V, 4.2 A, 148 Watt (L.V. side open) | |
| | | S.C test: 86 V, 10.5 A, 360 Watt (H.V. side shorted) | |
| | | Determine: (i) Regulation at full load and 0.8 lagging p.f. | |
| | | (ii) Power factor on Short circuit. | |
| Q.5 | (a) | | 03 |
| • | () | Ω and secondary resistance of 0.01 Ω Calculate total equivalent | |
| | | resistance referred to primary and secondary. | |
| | (b) | • • • | 04 |
| | (0) | explain. | UT |
| | (c) | Explain the direct load test for determination of voltage regulation | 07 |
| | (C) | and efficiency of transformer with necessary diagram. | U1 |
| | | OR | |
| 0.5 | (-) | | 02 |
| Q.5 | (a) | Write a note on – grounding transformer. | 03 |
| | (b) | | 04 |
| | | connections of 3-Phase transformer. | |
| | | (i) Dd6 | |
| | | (ii) Dy1 | |
| | (c) | Explain on load tan changing of transformer | 07 |

www.kilesikeankei.com