

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2019

Subject Code: 2131004

Date: 11/06/2019

Subject Name: Digital Electronics

Time: 02:30 PM TO 05:00 PM


Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1**
- (a) Represent following numbers in 8 Bit Binary representation: **03**
 (i) $(126)_{10}$ (ii) $(79)_{10}$ (iii) $(-128)_{10}$
- (b) State and explain De Morgan's theorems with truth tables. **04**
- (c) Do as directed. **07**
- i. Find 8 bit representation of $(-1)_{10} = (\text{_____})_2$
 - ii. Find $A + A'B = \text{_____}$.
 - iii. _____ and _____ can work as universal gates.
 - iv. Define term: Propagation Delay
 - v. By keeping one input HIGH, NAND gate can work as Inverter to second input. (T/F)
 - vi. Convert $(FFFF)_{16} = (\text{_____})_{10}$.
 - vii. Convert $(125.625)_{10} = (\text{_____})_2$.

 - Q.2**
- (a) Simply Boolean Function : $F = A'B'C + A'BC + AB'$. **03**
- (b) Find the Boolean Equation for following circuit and simplified Boolean equation. **04**



- (c) Draw logic circuit of Full Adder and Full Subtractor with truth table. **07**
- OR**
- (c) Generate AND, OR, NOT, EXOR and EX-NOR gate using NAND as a universal gate. **07**

- Q.3**
- (a) Obtain canonical Sum of Product form of following function: $F = AB + ACD$. **03**
- (b) Draw logic circuit of 2x4 Decoder. **04**
- (c) Simply Boolean function for $F(W,X,Y,Z) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ **07**

OR

- Q.3**
- (a) Explain working of Half Adder circuit with diagram. **03**
- (b) Draw logic circuit for 2-Bit Magnitude Comparator. **04**
- (c) Design 1-Bit Full Adder using 3x8 Decoder. **07**

- Q.4 (a) How to generate 8x1 MUX using 4x1 MUX. **www.FirstRanker.com** **www.FirstRanker.com** **03**
(b) Draw the circuit diagrams and Truth table of all the Flip flops (SR, D). **04**
(c) Derive and draw logic circuit for BCD to Excess-3 Code converter. **07**

OR

- Q.4 (a) Draw logic diagram, graphical symbol and Characteristic table for clocked T flip-flop. **03**
(b) Explain 4-Bit serial in serial out shift register. **04**
(c) Explain working of master-slave JK flip-flop with necessary logic diagram, state equation and state diagram. **07**
- Q.5 (a) Give comparison of TTL and CMOS family. **03**
(b) Draw and explain Ring counter. **04**
(c) Design synchronous counter for sequence: 0→1→3→4→5→7→0 using T flip-flop. **07**

OR

- Q.5 (a) What is race around condition in JK flip flop? **03**
(b) Write short note on Programmable Logic Arrays. **04**
(c) Explain the Fundamental Mode Model of Asynchronous State Machine with suitable example. **07**

www.FirstRanker.com