

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (New) EXAMINATION – WINTER 2018

Subject Code:2131704

Date:05/12/2018

Subject Name: Digital Logic Circuits

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Design 3 to 8 line decoder with neat sketch and truth table. **03**
 (b) Explain ROM with block diagram. Give classification of ROM. **04**
 (c) Explain D type edge triggered flip flop in detail. **07**
- Q.2** (a) Design full subtractor with necessary derivation of functions. **03**
 (b) What do you mean by universal gates? Implement NOT, AND, OR with both universal gates. **04**
 (c) Design 3 bit binary counter using T flip flops. **07**
- OR**
- (c) What is the limitation of Clocked RS flip flop? How it can be resolved using J K flip flop. **07**
- Q.3** (a) Explain gray code in detail. **03**
 (b) Express the boolean function $F = xy + x'z$ in a product of maxterm form. **04**
 (c) Design 4 bit bidirectional shift register with parallel load facility. **07**
- OR**
- Q.3** (a) Give the comparison of 1's and 2's complements. **03**
 (b) Show that $AB'C + B + BD' + ABD' + A'C = B + C$ **04**
 (c) Design BCD ripple counter. **07**
- Q.4** (a) Convert $(163.875)_{10}$ to binary. **03**
 (b) Explain duality principle with suitable example. **04**
 (c) Explain arithmetic, logic and shift microoperations. **07**
- OR**
- Q.4** (a) Subtract $(111.111)_2$ from $(1010.01)_2$ **03**
 (b) Explain DeMorgan theorem with suitable example. **04**
 (c) Explain emitter coupled logic with neat sketch. **07**
- Q.5** (a) Simplify the Boolean expression $F(A,B,C,D) = \Sigma(2,3,6,7,8,10,11,13,14)$ using K Map. **03**
 (b) Simplify the Boolean function $F(w,x,y,z) = \Sigma(1,3,7,11,15)$ with don't care condition $d(w,x,y,z) = \Sigma(0,2,5)$ **04**
 (c) Explain dual slope analog to digital converter. **07**
- OR**
- Q.5** (a) Simplify Boolean function $F = A'B'C' + B'CD' + A'BCD' + AB'C'$ using K map. **03**
 (b) Reduce the following expressions $F_1(A,B,C,D) = \Sigma(1,2,3,6,8,12,14,15)$ and $F_2(A,B,C,D) = \Pi(0,4,9,10,11,14,15)$ using K map. **04**
 (c) Explain R-2R ladder type digital to analog converter. **07**
