

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (OLD) EXAMINATION – WINTER 2018

Subject Code:141101**Date: 05/12/2018****Subject Name: Advance Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Draw hybrid π equivalent circuit for common emitter transistor. Also derive the expression for input conductance ($g_b'e$).	07
	(b) What is feedback? List the advantages of negative feedback. Derive relation between gain with and without feedback in a transistor amplifier.	07
Q.2	(a) Explain briefly the following terms: (1) Virtual Ground concept of OP-AMP (2) "Barkhausen criteria" for oscillator circuit.	07
	(b) Draw hybrid π circuit for a single stage CE transistor amplifier having load resistance R_L and obtain expression for short-circuit current gain and bandwidth.	07
OR		
	(b) Define the following terms: : (1) Common Mode Gain (2) Differential Gain (3) PSRR (4) Noise margin (5) fan-out (6) Common Mode Rejection Ratio (7) Figure of merit for logic families	07
Q.3	(a) Three cascaded stages amplifier have an upper 3 dB frequency of 16 KHz and a lower 3 dB frequency of 25 Hz. What are the values of f_L and f_H of each stage? Assume that all the stages are identical. Also calculate the bandwidth of each stage.	07
	(b) Explain in detail two stages RC coupled amplifier with its frequency response.	07
OR		
Q.3	(a) For the voltage amplifier $A_v = 140$, $f_L = 200$ Hz, $f_H = 200$ KHz, $R_i = 2K\Omega$, $R_o = 4.7K\Omega$. When negative feedback is employed in it with $\beta = 0.4$, determine the A_{vf} , R_{if} , R_{of} , F_{LH} , F_{HF} .	07
	(b) Explain important characteristics of ideal Op-Amp.	07
Q.4	(a) Draw the symbol and AC equivalent circuit of a Crystal oscillator and explain the principle of operation of Crystal Oscillator.	07
	(b) What is the significance of CMRR? List and explain the methods to improve the CMRR.	07
OR		
Q.4	(a) Draw the equivalent circuit of a practical OP-AMP and explain the significance of each component shown in it.	07
	(b) Draw op-amp based Wien bridge oscillator. Obtain frequency of oscillation and discuss amplitude stabilization for the same.	07

- Q.5 (a) What is Digital to Analog Converter? Draw and Explain R-2R DAC? Also give the advantages and disadvantages of R-2R Digital to Analog convertor. **07**
- (b) Explain in detail two input TTL-NAND Gate (Totempole Output) **07**
- OR**
- Q.5 (a) Tabled the compare of TTL, CMOS, and ECL logic families based on speed, fan-in, fan-out, noise immunity, power dissipation, and application. **07**
- (b) Explain working of successive approximation ADC with block diagram. **07**

www.FirstRanker.com