

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-V (OLD) EXAMINATION – WINTER 2018****Subject Code:151006****Date: 30/11/2018****Subject Name: Applied Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What is regulated power supply? Draw and explain block diagram of SMPS. **07**  
Also write advantage of SMPS.
- (b) Draw the block diagram of an OP-AMP and explain the function of each block. **07**
- Q.2** (a) Draw and explain block diagram of IC 555. Also explain the Pin connection of IC 555. **07**
- (b) Write short note on CRO. **07**
- OR**
- (b) Explain Ideal characteristics of operational amplifier. **07**
- Q.3** (a) Explain half adder and full adder circuit using logic diagram. **07**
- (b) Explain Astable multivibrator. **07**
- OR**
- Q.3** (a) What is LVDT? Explain principle and operation of LVDT. Also list the advantage and application of LVDT. **07**
- (b) Explain monostable multivibrator. **07**
- Q.4** (a) What is SCR? With required figure explain the operation and I-V characteristics of SCR. **07**
- (b) What is an optocoupler/optoisolator? Explain any one application of the same. **07**
- OR**
- Q.4** (a) Explain construction and working of UJT. Also explain UJT as relaxation oscillator. **07**
- (b) What is TRIAC? Draw and explain the construction of TRIAC? Also explain its operation. **07**
- Q.5** (a) What is sequential circuit? Explain any one sequential circuit with necessary circuit diagram in detail. **07**
- (b) Explain architecture of 8051 with block diagram. **07**
- OR**
- Q.5** (a) Write short note on Photocopier machine. **07**
- (b) What is Bar Code Scanner? Draw and explain the operation of Bar Code Scanner with required figure. **07**

\*\*\*\*\*