

Seat No.: _____


Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-V (OLD) EXAMINATION – WINTER 2018****Subject Code:152401****Date: 04/12/2018****Subject Name: Power Electronics Devices & Components****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks
4. Notation/Symbols have used meaning.

Q.1 (a) Draw the symbol and V-I Characteristics of the following : **08**
(i) LASCR (ii) GTO (iii) UJT (iv) TRIAC.

(b) **06**

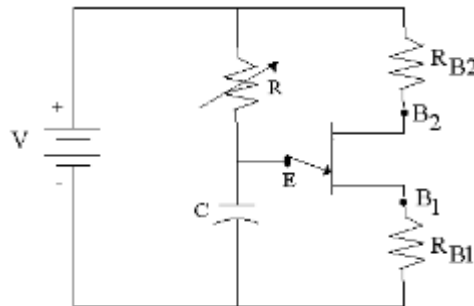

Analyze the working of the circuit shown in fig1.

Q.2 (a) State requirements for successful commutation. Explain class A commutation method for thyristor. **07**

(b) Discuss ideal switch characteristics. Enlist various types of losses in an electronic switch **07**

OR

(b) Discuss the various Turn-on methods for Thyristor.

Q.3 (a) Describe reverse recovery characteristics of a diode with necessary diagram(s). **07**

(b) Sketch symbol and equivalent circuit of depletion type Power MOSFET. Describe its operation in detail. **07**

OR

Q.3 (a) Describe the principle of operation of a Schottky Diode. State its applications. **07**

(b) Enlist various driving circuit used for Power BJT and discuss any one of them. **07**

Q.4 (a) Write short note on:- (i) Opto-coupler (ii) PiN diode **07**

(b) Explain cooling & mounting techniques for a power device in detail. **07**

OR

Q.4 (a) Discuss switching characteristic of an IGBT. **07**

(b) Enlist factors responsible for un-reliable operation of a thyristor. Discuss remedies for any two of them. **07**

- Q.5** (a) Discuss parallel operation of two Power MOSFETs. **07**
(b) Draw and explain two transistor model of an SCR. **07**

OR

- Q.5** (a) Write notes on: - (i) SITH (ii) MCT. **07**
(b) Compare Power MOSFET with SCR for various aspects. **07**

www.FirstRanker.com