

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2018****Subject Code: 2170808****Date: 26/11/2018****Subject Name: Sensor Networks & Instrumentation****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain sensors parameter. **03**
(b) Explain humidity sensors in details. **04**
(c) Explain Second Order Band Pass Filter in detail **07**
- Q.2** (a) Explain loading effect on sensors output. **03**
(b) Explain KRC filters equations. **04**
(c) Explain with neat sketch CO₂ Sensing techniques with necessary equations and graphs. **07**
- OR**
- (c) Explain Transducer Bridge Amplifier using Op-Amp with Application **07**
- Q.3** (a) Explain characteristics of an Ideal OP-AMP. **03**
(b) Explain advantages of smart sensors. **04**
(c) How to select a sensor? Explain selection of sensor in detail **07**
- OR**
- Q.3** (a) What is Negative Feedback? **03**
(b) Explain Multiple Feedback filters. **04**
(c) Explain various factors influencing WSN design **07**
- Q.4** (a) What is wireless sensor network?. **03**
(b) Explain Zigbee Network **04**
(c) What is Sensor? Give classification of sensors with respect to various parameters. **07**
- OR**
- Q.4** (a) Explain First Order RC filters **03**
(b) Explain capacitive sensor. **04**
(c) Explain general architecture of smart sensor **07**
- Q.5** (a) Explain feedback system in OP-AMP circuit. **03**
(b) What is Negative Feedback? What are its advantages? **04**
(c) Explain first order low pass filter and derive all equations with neat figure. **07**
- OR**
- Q.5** (a) Explain KRC filters **03**
(b) Explain first order Low Pass active filter **04**
(c) Explain First Order RC filters and derive its equations. **07**
