

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2018****Subject Code: 2172410****Date: 03/12/2018****Subject Name: Power Electronics Design****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1**
- (a) Enlist various attributes of ideal gate drive circuits. **03**
 - (b) Draw the ideal shape of base drive pulse for power transistor and give circuit configuration to produce such a base drive signal. **04**
 - (c) Discuss the steps in engineering design process for power electronics with appropriate example **07**
- Q.2**
- (a) Explain the concept of snubber Circuit. **03**
 - (b) Discuss importance of isolation for gate drive circuit. **04**
 - (c) Discuss crow-bar protection scheme using SCR. **07**
- OR**
- (c) An inductor is having rectangular core with following dimensions: $A_g = A_c = 9 \text{ cm}^2$, $l_g = 0.05 \text{ cm}$, $l_c = 30 \text{ cm}$, $N = 500$, $\mu_r = 72300$ for core material. Find inductance L of the winding, Where c stands for core; g stands for air gap. **07**
- Q.3**
- (a) Explain multi-layer PCB in brief. **03**
 - (b) Explain Baker's Clamp Circuit with diagram and also discuss requirements of it in base driver circuit of Power Transistor. **04**
 - (c) Write a short note on SCR ratings. **07**
- OR**
- Q.3**
- (a) Derive the r.m.s value of current whose equation is given by $i(t) = 5 + 10 \cos(\omega t + 30^\circ)$. **03**
 - (b) Give significance of proportional base control drive and also draw the driver circuit for the same. **04**
 - (c) Enlist and explain the steps to design a transformer for line frequency power converters. **07**
- Q.4**
- (a) What is energy equation of inductor ? **03**
 - (b) Describe the isolated gate driver for SCR with pulse transformer. **04**
 - (c) Describe the function of PUT with suitable example circuit. **07**
- OR**
- Q.4**
- (a) Explain characteristics of UJT. **03**
 - (b) What is di/dt trouble for SCR ? Discuss remedies for the same. **04**
 - (c) Write a brief note on PCB designing **07**
- Q.5**
- (a) For a full wave rectifier minimum how many isolated power supplies will be required for driver circuits ? Justify your answer. **03**
 - (b) Describe the isolated base driver for MOSFET with opto-coupler IC. **04**

- (c) The maximum junction temperature of a bipolar junction transistor is $T_{jmax} = 150^{\circ}\text{C}$ and the maximum power dissipation is 2.0 W at ambient temperature $T_A = 25^{\circ}\text{C}$ and 40 W at case temperature $T_c = 25^{\circ}\text{C}$. Calculate the maximum allowable power dissipation of the transistor operating in ambient temperature of 50°C in free air environment. **07**

OR

- Q.5** (a) Compare active and passive heat sink. **03**
(b) Explain totem pole configuration of MOSFET drive circuit. **04**
(c) Give the concept of thermal resistance. Describe the analogy between thermal and Electrical quantities. **07**

www.FirstRanker.com