

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (OLD) EXAMINATION – WINTER 2018****Subject Code: 172401****Date: 29/11/2018****Subject Name: Power Electronics Systems Modelling****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What is the requirement of normalization? Explain normalization w.r.t. frequency. **07**  
(b) Explain the working of the buck converter with neat circuit diagram and necessary waveforms. Draw the graph for DC conversion ratio  $M(D)$  versus duty cycle. **07**
- Q.2** (a) What is mathematical modeling? Draw and explain the block diagram of Power Electronics System with reference to modeling. **07**  
(b) State and explain inductor voltage-second balance principle. **07**  
**OR**  
(b) State and explain capacitor charge balance principle. **07**
- Q.3** (a) Derive the state-space model of a Boost converter. **07**  
(b) Explain the difference between ideal and physical models of AC transformer. **07**  
**OR**
- Q.3** (a) Derive the state-space model of a Buck-Boost converter. **07**  
(b) Explain DC transformer model with necessary equations and figures. **07**
- Q.4** (a) Develop the model of a DC motor. **07**  
(b) Explain: Controllability, Observability and normalized model. **07**  
**OR**
- Q.4** (a) List and explain the major steps of engineering design process. **07**  
(b) What do you mean by small signal approximation? Explain with appropriate example. **07**
- Q.5** (a) Explain the modelling of PWM inverter. **07**  
(b) Discuss the objectives of AC modeling and the concept of non-linearity introduced due to switching. **07**  
**OR**
- Q.5** (a) Explain the state space model of a full bridge inverter. **07**  
(b) What is feed forward control? Explain the basic working concept and its requirement in a control loop. **07**

\*\*\*\*\*