

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (OLD) EXAMINATION – WINTER 2018****Subject Code:133402****Date:28/11/2018****Subject Name:Electrical Drives And Controls****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the classes of motor duty in details. **07**
(b) What is an electrical drive? Draw and explain the block diagram of electrical drives. Also write down its advantages? **07**
- Q.2** (a) Write a short note on various characteristics of DC shunt motor **07**
(b) A 4-pole, 240 V, wave connected shunt motor gives 1119 kW when running at 1000 rpm and drawing armature and field currents of 50 A and 1.0 A respectively. It has 540 conductors and its resistance is 0.1 ohms. Assuming a drop of 1 Volt per brush, find (1) total torque (2) useful torque (3) useful flux/pole (4) rotational losses and (5) Efficiency **07**
- OR**
- (b) A 250 V shunt motor with armature resistance of 0.5 Ω runs at 600 r.p.m on full load and takes an armature current of 20A. If resistance of 1.0 Ω is placed in the armature circuit, find the speed at (i) full load torque (ii) half full load torque. **07**
- Q.3** (a) State and explain the different classes of Squirrel cage motor. **07**
(b) Explain Split phase & Shaded pole Induction motor with a neat sketch. **07**
- OR**
- Q.3** (a) Describe in detail the braking of DC shunt motor with neat sketch. **07**
(b) Explain Autotransformer starter with neat diagram **07**
- Q.4** (a) What is the need of starter in DC motor? Explain 3-point starter with diagram **07**
(b) Describe the Ward-Leonard speed control method? **07**
- OR**
- Q.4** (a) Explain the speed control methods of three phase induction motor by **07**
(1) Stator voltage control
(2) Frequency control
(b) Explain the different slip power recovery schemes? **07**
- Q.5** (a) Explain types of Choppers with neat sketch. **07**
(b) Explain Single phase Full bridge inverter with Resistive load **07**
- OR**
- Q.5** (a) Explain V/F control for AC drives. **07**
(b) Explain Single phase Half wave controlled rectifiers with Resistive load. **07**
