

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2017****Subject Code: 2171707****Date: 02/11/2017****Subject Name: Industrial Drives and Control****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List out different selection criteria for the electrical drive. **03**  
(b) Obtain the state space model of the DC machine. **04**  
(c) Explain methods to measure the different DC machine constants. **07**

- Q.2** (a) Explain shunt motor with its torque-speed characteristics. **03**  
(b) A series operated DC machine has 1.5 HP, 220V, 1600 rpm, armature resistance of  $3\Omega$ , field resistance of  $1\Omega$ , frictional coefficient of 0.002 Nm/(rad/sec) and mutual inductance of 0.0675H. Find (i) air gap torque (ii) armature current (iii) armature voltage. **04**  
(c) The separately excited DC machine has rating of 1200 KW, 500V, 2200 A, 400 rpm with brush drop of 3V, field power 35KW and armature resistance of  $0.003\Omega$ . It has variable armature voltage and fixed field current. Derive (i) Frictional torque with frictional coefficient 10 Nm/(rad/sec) (ii) Back EMF constant (iii) Input power (iv) Efficiency. **07**

**OR**

- (c) Draw and explain equivalent circuit of DC machine. Derive the equation of electromagnetic torque. **07**
- Q.3** (a) Draw the waveforms of 1st quadrant chopper operation for DC motor drive. **03**  
(b) Explain closed-loop speed control using DC drives. **04**  
(c) Explain the half-wave controlled rectifier based drives of DC motor with necessary waveforms and derive output voltage equation. **07**

**OR**

- Q.3** (a) Explain principle of operation of the chopper. **03**  
(b) Draw the waveforms of 3rd quadrant chopper operation for DC motor drive. **04**  
(c) Explain with waveforms fully controlled rectifier based DC motor drive. **07**
- Q.4** (a) Explain multi-pulse modulation technique for the induction motor. **03**  
(b) Give properties of PWM waveforms. Explain PWM inverters. **04**  
(c) Explain PWM and HCC hysteresis chopper based closed operation of DC motor drive. **07**

**OR**

- Q.4** (a) Explain constant volts/Hz control for induction motor. **03**  
(b) Explain different input way to the chopper. **04**  
(c) Explain the operation of half-bridge modified McMurray inverter. **07**
- Q.5** (a) Draw and explain torque versus stepping rate characteristic of stepper motors. **03**  
(b) Explain construction and working of VR stepper motors. **04**  
(c) Explain brushless DC motor. **07**

- Q.5** (a) List out important features of the stepper motors.  
(b) Explain DC servo control.  
(c) Explain drive circuits for the stepper motors.

03

04

07

\*\*\*\*\*

www.FirstRanker.com