FirstRanker.com

www.FirstRanker.com

www.FirstRanker.com

	 	 	 	 	 	-

Total No. of Pages : 02

Total No. of Questions : 09

# B.Tech. (ECE) (Sem.-4,5) LINEAR INTEGRATED CIRCUITS Subject Code : EC-305 M.Code: 57521

Time: 3 Hrs.

Max. Marks: 60

## **INSTRUCTIONS TO CANDIDATES :**

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks 1. each.
- SECTION-B contains FIVE questions carrying FIVE marks each and students 2. have to attempt any FOUR questions.
- SECTION-C contains THREE questions carrying TEN marks each and students 3. have to attempt any TWO questions.

# **SECTION-A**

#### 1. Answer all the questions :

- Franker.com a. Draw the op-amp block diagram.
- b. Explain SVRR.
- c. Explain slew rate.
- d. Explain (MRR in OP-AMP.
- e. Draw the non- inverting op-amp circuit diagram.
- Define the terms linearity and accuracy of A/D convertors. f.
- g. List down the characteristics of ideal OP-AMP.
- h. What is the main advantage of constant current bias over emitter bias in differential amplifiers'?
- i. Define input-bias current in OP-AMP.
- Define capture range and lock-in range of a PLL. j.



www.FirstRanker.com

#### **SECTION-B**

- 2. Describe the Frequency Compensation techniques used in operational amplifier.
- 3. Explain the operation of ideal integrator using IC 741.
- 4. Draw the block diagram of averaging amplifiers and explain its operation in detail.
- Explain the operation of 1<sup>st</sup> order low pass filter along with circuit diagram. 5.
- 6. Explain the operation of a grounded load V to I converter using op-amp.

## **SECTION-C**

- 7. Explain triangular wave generator.
- 8. Explain the working of Schmitt trigger.
- 9. Write short notes on following
  - a. Wein bridge oscillator
- www.FirstRanker.com b. Summing and scaling amplifier

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any** page of Answer Sheet will lead to UMC against the Student.