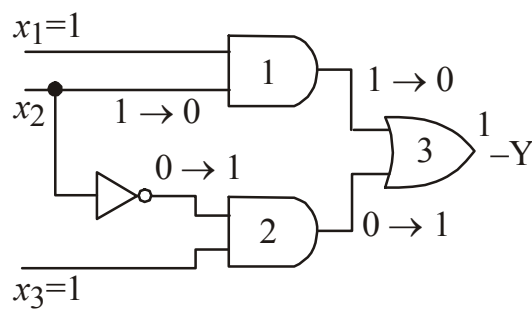


4. Differentiate Moore and Mealy machines.
5. Draw the block diagram of Asynchronous Sequential circuits and explain it.
6. Explain how to remove hazards? For a circuit shown below draw a hazards free circuit.



(a) AND-OR circuit


SECTION-C

7. A sequential circuit has two JK flip-flops A and B and one input x . The circuit is described by the following flip-flop input equations :

$$J_A = x \quad K_A = B$$

$$J_B = x \quad K_B = A'$$

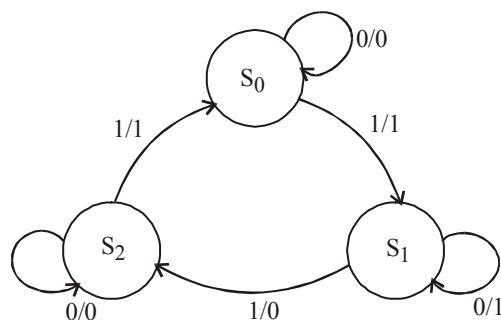- (a) Derive the state equations $A(t+1)$ and $B(t+1)$ by substituting the input equations for the J and K variables. (7)
- (b) Draw the state diagram of the circuit. (3)
8. Draw and explain the general structure of PLDs. Draw a simple four-input, three-output PAL derive. (7+3)
9. Convert the state diagram of Fig. below to ASM chart. (10)



NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.