

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Total No. of Pages : 03

Total No. of Questions : 09

B.Tech.(ECE) (2012 to 2017) / (Electronics & Telecom Engg.)
(Sem.-3)

NETWORK ANALYSIS AND SYNTHESIS**Subject Code : BTEC-303****M.Code : 57585****Time : 3 Hrs.****Max. Marks : 60****INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A**I. Answer briefly :**

- a) Differentiate between Network Analysis and Network Synthesis and state the methods to solve them.
- b) Define hybrid Parameters. Why they are called so?
- c) Find $F(t)$ if $F(s) = \frac{s+2}{(s+1)(s+5)}$.
- d) Explain different types of standard input signals with mathematical equations and diagram.
- e) Check the positive realness of

$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

- f) What are dependent and independent sources? List them and draw diagram.
- g) Differentiate between the properties of RC and LC circuits.
- h) Explain the difference between transient and steady state response.
- i) Define reciprocity theorem and state its applicability.
- j) Define convolution theorem of Laplace Transform.

SECTION-B

2. Find the current delivered to R_L using Thevenin theorem in Fig.1. Also verify your answer using Norton theorem.

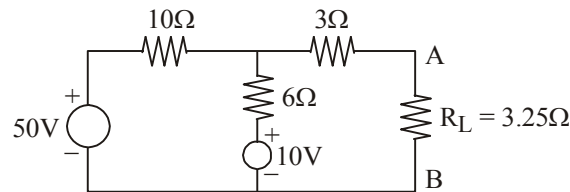


Fig.1

3. Find Y-parameters of the network of Fig. 2.

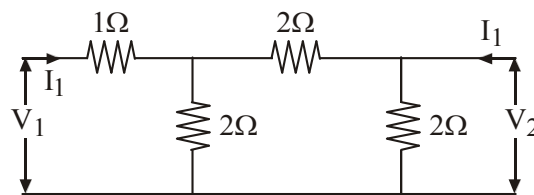


Fig.2

4. Steady state is achieved in the given circuit of Fig. 3. With switch, S open. Find the value of $I(t)$ for $t > 0$, if switch S is closed at $t = 0$.

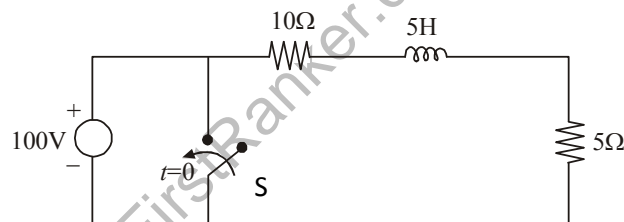


Fig.3

5. Using Mesh analysis, find I in the circuit of Fig. 4.

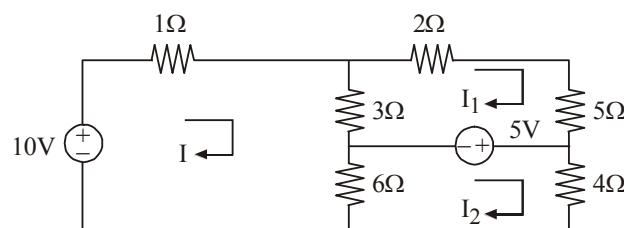


Fig.4

6. Classify filters and analyze any one type of filter in detail.

SECTION-C

7. Synthesize a network using foster-I and foster-II forms for the impedance function :

$$Z(s) = \frac{(s+1)(s+4)}{(s)(s+2)}$$

8. In the circuit shown in given Fig. 5, find the maximum power delivered to load R_L .

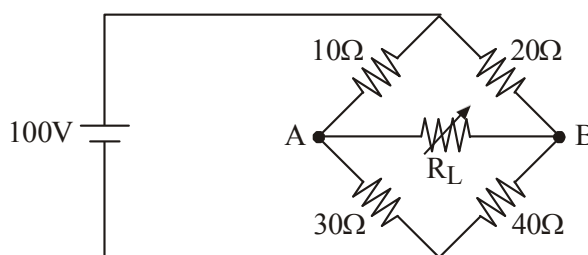


Fig.5

9. If a constant-K high pass filter has cut-off frequency of 10KHz and nominal impedance R_o is 700 Ω , design the T-and π -sections of this filter. Determine its characteristic impedance, phase constant at 25 KHz, and attenuation at 8KHz.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.