### www.FirstRanker.com

www.FirstRanker.com

Roll No. Total No. of Pages: 02

Total No. of Questions: 09

B.Tech.(EE) (2012 Onwards)/(Electrical & Electronics Engg.) (2011 Onwards)
B.Tech. (Electronics & Electrical Engg.) (2012 to 2017)

(Sem.-3)

# **CIRCUIT THEORY**

Subject Code: BTEE-301 M.Code: 57092

Time: 3 Hrs. Max. Marks: 60

#### **INSTRUCTIONS TO CANDIDATES:**

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- 2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
- 3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

#### **SECTION-A**

# 1. Answer briefly:

- a. Differentiate between periodic and singularity voltages.
- b. State Norton's theorem.
- c. What do you mean by doublet? Explain.
- d. What do you mean by transient response? Explain.
- e. Discuss the significance of circuit theory.
- f. What do you mean by singlet? Explain.
- g. What do you mean by propagation constant? Explain.
- h. Explain passband and stopband with respect to filters.
- i. What do you mean by the term composite filter? Explain.
- j. Why network synthesis is required? Explain.



#### **SECTION-B**

- 2. State and prove Maximum power transfer theorem.
- 3. What do you mean by pole and zero? Discuss its important features and restrictions.
- 4. Design T section of constant k high pass filter having nominal characteristic impedance of 600 ohm, cut-off frequency is 10 kHz. Also find its characteristics impedance and phase constant.
- 5. Define Laplace transform. Find the Laplace transform of sin ωt u(t-t0)
- 6. What is the need of a filter? Discuss the classification of filters in detail.

## **SECTION-C**

7. Find the Thevenin's and Norton's equivalent of the circuit shown in figure, at the terminals A & B.

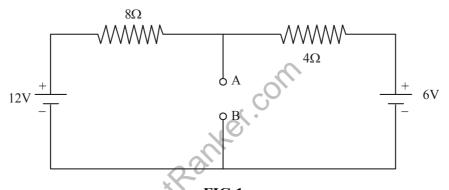


FIG.1

8. Find the first and second Foster or Cauer forms of the function:

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

- 9 Discuss the following
  - a. Convolution theorem
  - b. Design of m derived low pass filter

NOTE: Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

**2** M-57092 (S2)-835