

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(EE) PT (Sem.-3)

DIGITAL ELECTRONICS

Subject Code : BTEE-404

M.Code : 72164

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A

1. Answer briefly :

- (a) Convert $(7825.6875)_{10}$ to octal.
- (b) Multiply $(1010)_2$ by $(1011)_2$.
- (c) Simplify the Boolean expression: $\overline{(A+B)} \cdot \overline{(\overline{A} + \overline{B})}$
- (d) How much the number of cells in the Karnaugh map of a switching function (A,B,C) consisting of only three variables?
- (e) Differentiate between Flip-flop and latch.
- (f) To describe an entity, VHDL provides five different types of primary constructs, called design units, write the names of those primary constructs.
- (g) Differentiate between NMOS and PMOS logic family.
- (h) What is the conversion time of a 10 bit successive approximation A/D converter if its clock is 4 MHz?
- (i) Differentiate between static RAM and dynamic RAM.
- (j) Calculate the address lines required for an 8 K byte memory chip.

SECTION-B

2. Construct Hamming code for 1 0 1 1 1 0 0 1. Use odd parity.
3. Explain with the help of example, the Principle of Duality. Discuss its use in Boolean algebra.
4. Explain a general method for conversion from one type of flip-flop to another type.
5. Explain the entity declaration for the half-adder circuit.
6. Compare various characteristics of different types of A/D converters.

SECTION-C

7. Design a mod 12 ripple counter using J K flip-flops.
8. What is the basic principal reason why ECL logic is faster than TTL? Draw and explain DTL logic circuit.
9. Convert $4\text{ K} \times 8$ memory to $64\text{ K} \times 8$ memory.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.