### www.FirstRanker.com

www.FirstRanker.com

Roll No. Total No. of Pages: 02

Total No. of Questions: 09

B.Tech. (ECSE) (Sem.-7)
VLSI DESIGN
Subject Code: BTEC-604

M.Code: 72170
Time: 3 Hrs.

Max. Marks: 60

### **INSTRUCTIONS TO CANDIDATES:**

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- 2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
- 3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

### **SECTION-A**

# 1. Write briefly:

- a) State the advantages of VHDL.
- b) What is transport delay? How it differs from inertial delay?
- c) What is the range of natural and real data types in VHDL?
- d) How is generic statement useful in VHDL code?
- e) Differentiate between synthesis and simulation.
- f) Explain type declaration and its usage.
- g) Why NMOS technology is preferred more than PMOS technology?
- h) Differentiate enhancement mode and depletion mode transistors.
- i) Describe if else statement.
- j) What are various sources of power dissipation in CMOS circuits?



## **SECTION-B**

- 2) What are the different types of VHDL modeling? Explain with the examples.
- 3) Write the VHDL code for 3 bit Binary to Gray converter.
- 4) What is NMOS inverter? Discuss the transfer characteristics of it.
- 5) Explain pre-defined and user-defined attributes with the help of suitable examples.
- 6) What is scaling? What is the effect of scaling on the circuit performance?

## **SECTION-C**

- 7) Design and implement 16:1 Multiplexer using two 8:1 MUX and a logic gate in Verilog HDL.
- 8) Draw CMOS inverter and discuss its DC characteristics. Write the conditions for the different region of operations.
- 9) Write the VHDL code for 4-bit synchronous up counter using sequential statements.

NOTE: Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

**2** M-72170 (S2)-2759