

www.FirstRanker.com

www.FirstRanker.com

Subject	Title: Linear Integ	grated Circuits 8	Basics of	Communication
Year: II		Sen	nester: IV	

Prepared by: E Gayathri Updated on: 25/03/

Unit - I: Operational Amplifiers

- 1. Define operational amplifier.
- 2. Define the terms CMRR, Slew rate Virtual ground, Offset errors.
- 3. What are the ideal characteristics of op-amp?
- 4. Explain the need for differential amplifier.
- Discuss about Op-amp as differentiator, Integrator circuits. 5.
- 6. Draw the block diagram of operational amplifier and explain in detail.
- Explain the working of emitter coupled differential amplifier. 7.
- Discuss the working of operational amplifier as a summing amplifier and obtain the its 8. output voltage.
- 9. Draw the circuit diagram of inverting and non -inverting amplifiers and explain their operation. Derive expressions for voltage gain.
- 10. Explain the comparator action of an op-amp.
- 11. Describe how op-amp is used as a Voltage follower.
- ercorr 12. Discuss the working of op-amp as Subtractor.
- 13. Problems based on all topics.

Unit - II: Applications of operational amplifiers

- 14. Draw the block diagram of IC-555 timer and describe its working.
- 15. Draw the circuit of Astable Multivibrator with IC -555 and explain.
- 16. List out the features of 555 timer.
- 17. Draw the circuit of Wein bridge oscillator with op-amp and obtain its frequency.
- 18. Explain how op-amp can be as a logarithmic amplifier with a diode.
- 19. With the help of a neat diagram explain how op-amp is used to generate a sine wave?
- 20. Draw the circuit diagram of a square Wave generator using op-amp and explain its operation.
- 21. Draw the circuit of Triangular wave generator using op-amp and explain
- 22. Explain the working of Monostable multivibrator using op-amp.
- 23. Explain with a neat diagram, how op-amp can be used to solve differential equations of second order.
- 24. Explain with relevant diagrams, how IC-555 timer is used as astable multivibrator.
- 25. Explain with the help of a circuit diagram how IC-555 timer is used as a monostable multivibrator.



www.FirstRanker.com

- 26. What is Modulation?
- 27. What is the need for modulation?
- 28. Give advantages of AM.
- 29. Define modulation index of AM signal.
- 30. Derive the expressions for frequency spectrum of A.M wave.
- 31. What is AM? Show that an AM wave contains a carrier and two side bands for every modulating frequency.
- 32. Give the theory and working of diode detector to detect the AM signals.
- 33. Define Demodulation.
- 34. Explain the working of a simple amplitude modulator with relevant circuits.
- 35. Derive the expressions for total transmitted power of AM wave.
- 36. Explain the working of Balanced modulator circuit.
- 37. Explain the principle of AM detection and classify A.M. detectors.
- 38. Draw the circuit of envelop diode detector and explain graphically the conditions.
- 39. Draw the circuit diagram of square law diode modulator and explain its performance.
- 40. Problems based on all topics.

Unit - IV: Frequency modulation

- 41. Define frequency modulation.
- 42. Write the expressions for band width of FM Signal
- 43. Give the advantages and disadvantages of FM.
- 44. Draw the block diagram of FM radio receiver. Explain the Significance of each block.
- 45. Write about Delta modulation.
- 46. Write about PAM, PCM?
- 47. Give the Analysis of Frequency modulation.
- 48. Compare AM and FM.
- 49. Draw the circuit of simple frequency modulator and explain its working.
- 50. Draw the block diagram of Super hetero dyne receiver and explain its working .
- 51. Explain the principle and working of ratio detector.
- 52. Derive the expression for spectrum of F.M. Wave.
- 53. Explain how FM waves are detected?
- 54. Give an account of classification of pulse modulation techniques.
- 55. Draw the block diagram of FM discriminator with circuit diagram.
- 56. Problems based on all topics.