

www.FirstRanker.com

www.FirstRanker.com

Total No. of Questions: 18

B.Tech. (Electrical & Electronics) (2013 & Onwards E-II)/

B.Tech. (Electronics & Electrical) (Sem.-7)

HIGH VOLTAGE DIRECT CURRENT TRANSMISSION

Subject Code : BTEEE-804B M.Code : 71964

Time: 3 Hrs. Max. Marks: 60

INSTRUCTIONS TO CANDIDATES:

- SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
- SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

Write briefly:

- What is the difference between AC and DC transmission?
- What are the applications of DC transmission?
- Define the overlap angle and extinction angle.
- 4. What are the different types of modes of operation of rectifier?
- 5. What are the different HVDC links normally adopted?
- What are the applications of HVDC transmission system in India?
- 7. What are the possible reasons of over voltage occurrence in converter?
- 8. How do you fix transient overvoltage?
- 9. What is proximity effect in transmission lines?
- 10. What is the function of smoothing reactor?

1 | M-71964 (S2)-724





SECTION-B

- Discuss the working of monopolar operation of HVDC system.
- Discuss the application of Thyristor valve for HVDC transmission system.
- Analyze the working of Graetz circuit with overlap.
- 14. Draw the complete converter control characteristics and explain the principle of power control in a DC link.
- Discuss in detail about the modern HVDC converters.

SECTION-C

- Described about starting and stopping of DC link.
- Describe the working of over current and over voltage protection in a converter station.
- pulse conve 18. What is 12-pulse converter? Explain the 12 pulse converter operation.

NOTE: Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

2 | M-71964 (S2)-724

