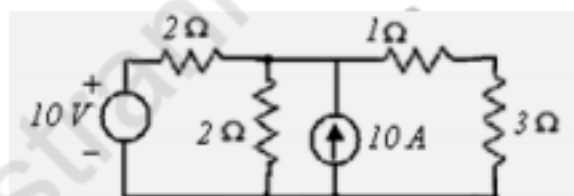


B.TECH.
THEORY EXAMINATION (SEM-II) 2016-17
BASIC ELECTRICAL ENGINEERING
Time : 3 Hours
Max. Marks : 100
Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.
SECTION – A
1. Explain the following:
10 x 2 = 20

- (a) Define unilateral and bi-lateral elements.
- (b) What are the advantages of three phase system over the single phase system?
- (c) Why the series resonance is called the voltage resonance?
- (d) What do you understand by an acceptor and rejector circuit?
- (e) Why damping torque is necessary for an analog type instruments?
- (f) What do you know about phase sequence in a three phase supply system?
- (g) How hysteresis loss can be minimised in a transformer?
- (h) Write the function of commutator in a DC generator.
- (i) Name any two motors, which can be used for purpose of constant speed.
- (j) Why condenser is necessary to be connected in ceiling fan?


SECTION – B
2. Attempt any five parts of the following questions:
5 x 10 = 50

- (a) Find the current in 3 ohm resistance by loop current method and verify the answer by node voltage method.



- (b) For the parallel circuit shown in figure, calculate the following;

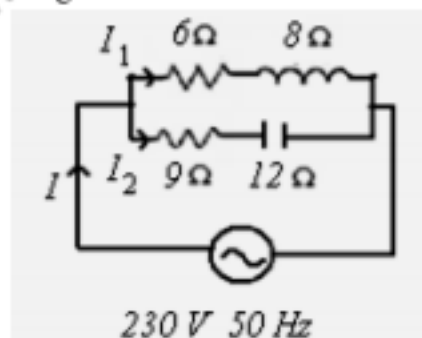- (i) Current through each branch
- (ii) Total current drawn and power factor of complete circuit.
- (iii) Equivalent impedance of the circuit.
- (iv) Draw phasor diagram



- (c) Define power factor? What are causes and effects of low power factor? What are the methods to improve the power factor of an ac circuit?
- (d) A Series R-L-C circuit consists of a resistance of 10Ω an inductance of $0.1H$ and a capacitance of $8\mu f$. Determine;
 - (i) the resonance frequency,
 - (ii) the Q factor of the circuit at resonance,
 - (iii) Band-width
 - (iv) the half power frequencies


- (e) What are the power losses in a transformer? Define efficiency and obtain the condition for a transformer, when it operates at its maximum efficiency.
- (f) Explain construction and working of attraction type moving iron instrument. List the advantages and disadvantages of these instruments.
- (g) A 20 KW, 250V dc shunt machine has armature and field resistances 0.1 ohm and 125 ohm respectively. Calculate the emf developed in armature when running (i) as a generator delivering 20 KW output (ii) as a motor taking 20 KW input.
- (h) Write the working principle of a three phase induction motor. Draw its torque-slip characteristics and show operating, breaking and generating regions of motor.

SECTION – C

Attempt any two of the following questions:

2 x 15 = 30

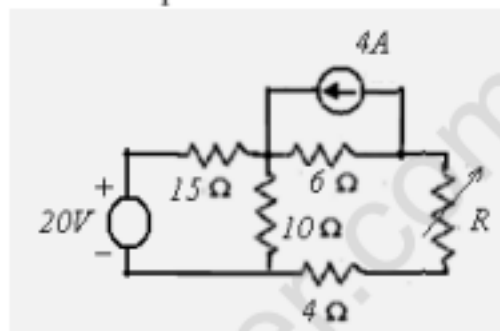3. (a) State and prove maximum power transfer theorem.
 (b) Find the value of resistance R for maximum power transfer in the circuit shown. Also obtain the value of maximum power.



4. (a) Discuss the Quality factor and Bandwidth in detail.
 The power of a 400 volts, 3-phase, star connected 3-phase circuit is measured by two-wattmeter method. If the readings of both wattmeter's are found to be 50 kW and 30 kW, then calculate the followings;
 (i) Circuit power factor
 (ii) Total active and reactive power.
 (iii) Line current drawn by the circuit.
 (iv) Impedance per phase.
5. (a) A moving coil instrument gives a full scale deflection of 20 mA when a potential difference of 50 mV is applied. Calculate the series resistance to measure 500 V on full scale.
 (b) Explain double field revolving theory.
 (c) Write applications of three phase synchronous motor.