

B.TECH.
THEORY EXAMINATION (SEM-II) 2016-17
BASIC ELECTRONICS
Time : 3 Hours
Max. Marks : 70
Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.
SECTION – A
1. Explain any seven of the following:
7 x 2 = 14

- Classify the materials with help of energy band.
- Explain the principle of operation of LED.
- Derive the relationship between α and β .
- Why are FET called unipolar device?
- Write down the constructional difference between Depletion type and Enhancement type MOSFET.
- Derive the circuit of integrator using an ideal Op-Amp.
- State the advantages of digital instruments over analog instruments.
- Briefly discuss the need of modulation in communication engineering.

SECTION – B
2. Attempt any five of the following questions:
5 x 7 = 35

- Explain the V-I characteristic of p-n junction diode. How it is differ from Zener diode?
- Draw the circuit and discuss the working of full wave bridge rectifier with suitable input -output waveforms. What is PIV of bridge rectifier?
- Draw and explain the construction and working of p-channel depletion type MOSFET. Also draw the characteristics of p-channel depletion type MOSFET.
- Calculate the output voltage for the circuit of Figure 1 with inputs of $V_1 = 40$ mV rms and $V_2 = 20$ mV rms.

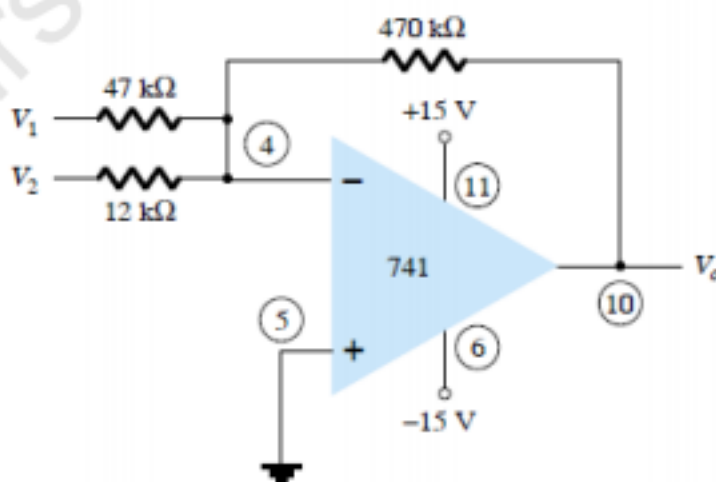


Figure 1

- Given that $I_{CQ} = 2$ mA and $V_{CEQ} = 10$ V, determine R_1 and R_C for the network of Figure2.

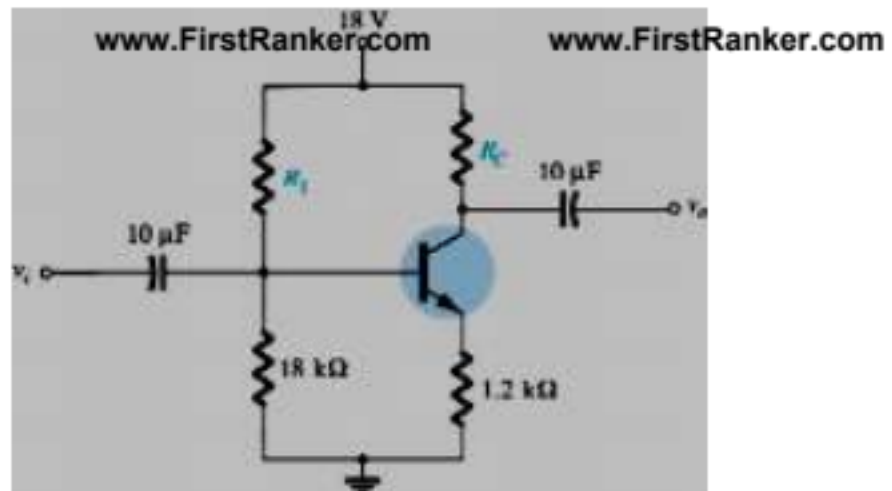


Figure 2

- (f) Draw and explain the block diagram of Ramp type digital voltmeter. Also draw related voltage to time conversion waveforms.
- (g) Derive the expression for AM modulated waveform. Also derive the expression for modulation index.
- (h) Describe the operation of CRT with neat block diagram. How unknown frequency is measured using CRO?

SECTION – C

Attempt any two of the following questions:

2 x 10.5 = 21

3. (a) Explain principle of operation and construction of Tunnel diode. Draw its V-I characteristic.
- (b) Design a clamper to perform the function indicated in Figure 3.

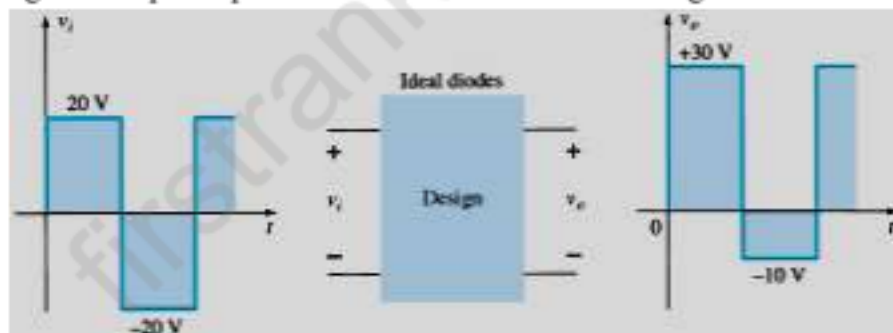


Figure 3

4. (a) Draw and explain the N-channel JFET and draw its transfer characteristics.
- (b) Draw and explain the differential amplifier. Define CMRR and slew rate in Op-Amp.
5. (a) Draw the CE n-p-n BJT characteristics. Also explain the self bias configuration in DC bias configuration.
- (b) Discuss the need of modulation in the communication engineering. Which types of modulations are used in television?