

NEC - 304

- h) Compare mealy and Moore model of finite state machine.
- i) The contents of a four bit register are initially 1011. The register is shifted six times to the right with serial input being 101111. What are the contents of the register after each shift?
- j) Write the steps that must be taken for the purpose of transferring a new word to be stored into memory.

Section - B

Attempt any five questions from this section

(5×10=50)

- a) Simplify the Boolean function.

$$F(w,x,y,z) = \sum(1,3,7,11,15)$$
 Which has the don't care conditions

$$d(w,x,y,z) = \sum(0,2,5)$$
- b) Implement the following Boolean function with NAND gates

$$F(x,y,z) = \sum(1,2,3,4,5,7)$$
- c) Design a full subtractor circuit with three inputs x, y, B_{in} and two outputs Diff and B_{out} . The circuit subtracts $x-y-B_{in}$, where B_{in} is the input borrow, B_{out} is the output borrow and Diff is the difference.
- d) Draw the logic diagram of a two to four line decoder using NOR gates only.

104/12/2016/6700

(2)

NEC - 304

- e) Construct a JK flip-flop, using a D flip-flop, a two to four one line multiplexer and an inverter.
- f) Design a hazard free circuit for the following Boolean function $F(x_1, x_2, x_3) = \sum(1, 5, 6, 7)$
- g) Describe the operation of four bit synchronous binary counter with neat sketch.
- h) Draw the basic configuration of three PLDs.

Section - C

Note: Attempt any two questions from this section.

(2×15=30)

3. Minimize the following switching function using Quine-McCluskey method

$$F(x_1, x_2, x_3, x_4, x_5) = \sum(0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$$
4. Design a combinational circuit that converts a BCD code to Excess-3 code.
5. Implement the following four boolean functions with a PAL.

$$W(A, B, C, D) = \sum(2, 12, 13)$$

$$X(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$Y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$Z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

304/12/2016/6700

(3)