

Printed Pages: 3

NEC - 304

(Following Paper ID and Roll No. to be filled in your Answer Books)

Paper ID : 2289462

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.TECH.

Regular Theory Examination (Odd Sem - III), 2016-17
SWITCHING THEORY AND LOGIC DESIGN

Time : 3 Hours

Max. Marks : 100

Section - A

1. Attempt all parts. All parts carry equal marks. Write answer of each part in short (10×2=20)
- a) Convert $(153.513)_{10}$ to an octal number
 - b) Write the advantages of gray code over the straight binary number sequence.
 - c) Give the general procedure for converting a multilevel AND-OR diagram into an all NAND diagram.
 - d) Draw the logic diagram of half subtractor
 - e) Specify the purpose of valid bit indicator in priority encoder.
 - f) Give the function table of SR latch.
 - g) Express the characteristic equation for the JK flip-flop.

304/12/2016/6700

(1)

PTC

NEC - 304

- h) Compare mealy and Moore model of finite state machine.
- i) The contents of a four bit register are initially 1011. The register is shifted six times to the right with serial input being 101111. What are the contents of the register after each shift?
- j) Write the steps that must be taken for the purpose of transferring a new word to be stored into memory.

Section - B

Attempt any five questions from this section

(5×10=50)

- a) Simplify the Boolean function.
 $F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$
Which has the don't care conditions
 $d(w, x, y, z) = \sum(0, 2, 5)$
- b) Implement the following Boolean function with NAND gates
 $F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$
- c) Design a full subtractor circuit with three inputs x, y, B_{in} and two outputs Diff and B_{out} . The circuit subtracts $x - y - B_{in}$, where B_{in} is the input borrow, B_{out} is the output borrow and Diff is the difference.
- d) Draw the logic diagram of a two to four line decoder using NOR gates only.

104/12/2016/6700

(2)

NEC - 304

- e) Construct a JK flip-flop. using a D flip-flop. a two to four one line multiplexer and an inverter.
- f) Design a hazard free circuit for the following Boolean function $F(x_1, x_2, x_3) = \sum(1, 5, 6, 7)$
- g) Describe the operation of four bit synchronous binary counter with neat sketch.
- h) Draw the basic configuration of three PLDs.

Section - C

Note: Attempt any two questions from this section.

(2×15=30)

- 3. Minimize the following switching function using Quine-McCluskey method
 $F(x_1, x_2, x_3, x_4, x_5) = \sum(0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$
- 4. Design a combinational circuit that converts a BCD code to Excess-3 code.
- 5. Implement the following four boolean functions with a PAL.
 $W(A, B, C, D) = \sum(2, 12, 13)$
 $X(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$
 $Y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$
 $Z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$

304/12/2016/6700

(3)