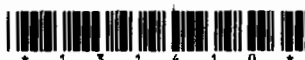


Printed Pages : 3



NEC409(A)

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 131410**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. IV) THEORY EXAMINATION, 2014-15  
**ANALOG AND DIGITAL ELECTRONICS**

Time : 3 Hours]

[Total Marks : 100

- 1 Attempt any four parts : 5×4=20
- (a) Discuss how the variable capacitance is achieved in varactor diode. Enlist the application of varactor diode.
  - (b) Explain the principle and working of light emitting diode (LED) with V-I characteristics.
  - (c) Draw the V-I characteristics of tunnel diode and indicate the useful region in the curve.
  - (d) Draw the output characteristics of transistor and also explain how it is used as a switch.
  - (e) An LED is connected across a voltage source of +10V through a series resistance of  $820\ \Omega$ . Calculate the LED current. Assume the voltage drop across an LED of 15 Volt.
  - (f) Define the following terms :
    - (i) Rise time
    - (ii) Fall time
    - (iii) Delay time
    - (iv) Storage time.

131410]

1

[ Contd...

2 Attempt any four parts : **5×4=20**

- Derive the input and output resistance of a Transconductance and Voltage amplifier.
- Calculate the voltage gain, input and output resistance of voltage series feedback amplifier having  $A_v = 300$ ,  $R_i = 1.5k \Omega$ ,  $R_o = 50k \Omega$  and  $\beta = 1/15$ .
- Describe the properties of series-shunt and shunt-shunt feedback amplifier.
- Draw the high frequency equivalent circuit or the typical RC coupled common emitter amplifier.
- An RC coupled amplifier has voltage gain of 1000,  $f_1 = 50 \text{ Hz}$ ,  $f_2 = 200 \text{ kHz}$  and a distortion of 5% without feedback. Find the amplifier voltage gain,  $f_1$ ,  $f_2$  and distortion when negative feedback is applied with feedback ratio 0.01.
- List five characteristics of an amplifier which are modified by negative feedback.

3 Attempt any two parts : **10×2=20**

- Discuss how does the circuit of a hartley oscillator differ from that of a Colpitt oscillator.
  - Explain the properties of a quartz crystal which are responsible for its use in oscillator.
- What is the Barkhausen criterion for the Feedback oscillator? Draw a neat diagram of phase shift oscillator using BJT. Derive an expression for its frequency of oscillation.
- A coupling oscillator is designed with  $C_1 = 100 \text{ pF}$  and  $C_2 = 7500 \text{ pF}$ . The inductance is variable. Determine the range of inductance values, if the frequency of oscillation is to vary between 950 kHz and 2050 kHz.

4 Attempt any two parts : **10×2=20**

- Implement the following Boolean function using 8:1 multiplexer  
 $F(A,B,C,D) = \sum (2,4,5,7,10,14)$
  - Explain the working of SR flip-flop using NAND gates.
- Differentiate between an encoder and decoder.
  - Tabulate the excitation table of J-K flip flop.
- Draw and explain the working of 4-bit up and down synchronous counter. Also describe the working of shift register.

5 Attempt any two parts : **10×2=20**

- Explain the organisation of RAM with the help of neat diagram. Also describe the switching regulators.
- Explain A/D convertor using voltage to frequency convertor. Describe any one method of A/D convertor.
- What are the voltage regulators? Discuss the working of shunt and series op-amp based voltage regulators.

131410] 2 [Contd...

131410] 3 [17425]