

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131406

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. IV) THEORY EXAMINATION, 2014-15
ELECTRONIC CIRCUITS

Time : 3 Hours]

[Total Marks : 100

Note: (1) Attempt all questions.

(2) All questions carry equal marks.

1 Attempt **any four** parts of the following:- **5×4=20**

- Draw the circuit diagram of difference amplifier using OP-AMP and calculate the differential gain (A_d) and differential input resistance (R_{id}).
- For the circuit in Fig.(1) calculate the values of v_1 , i_1 , i_2 , v_o , i_L and i_o . Also calculate the voltage gain, current gain and power gain.

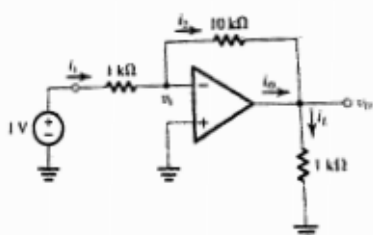


Fig.(1)

1

[Contd...

131406]

(e) An inverting amplifier with nominal gain of -20V/V employs an op-amp having a dc gain of 10^4 and a unity gain frequency of 10^6Hz . What is the 3-dB frequency f_{3dB} of the closed loop amplifier? What is the gain at $0.1 f_{3dB}$ and at $10f_{3dB}$?


(f) (i) Describe the terms Unity-gain Bandwidth and Full-power Bandwidth.

(ii) For an op-amp having a slew rate of $60\text{V}/\mu\text{s}$, what is the highest frequency at which a 20-V peak to peak sine wave can be produced at the output.

2 Attempt any four parts of the following:- **5×4=20**

(a) Derive the i_D - V_{DS} relationship for NMOS working in saturation region

1314061 2 1 Contd...

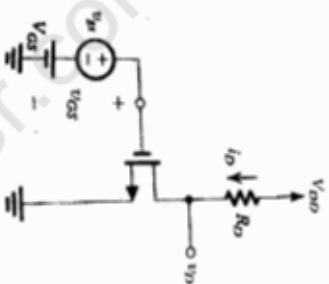

Fig(2)

(i) Find the dc quantities I_D and V_D

(ii) Calculate the value of g_m at the bias point.

(iii) Calculate the value of voltage gain.

(iv) If the MOSFET has $\lambda = 0.001\text{V}^{-1}$, find r_o at the bias point and calculate the voltage gain

1314061 3 1 Contd...

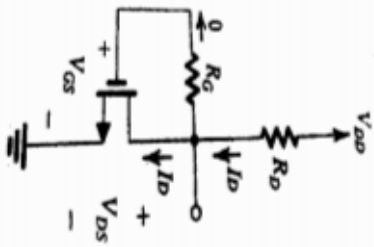


Fig. (3)

- (i) Calculate the overall gain $G_v = V_o/V_{sig}$, input resistance and output resistance for a Common Source Amplifier.

1314061

4

[Contd...

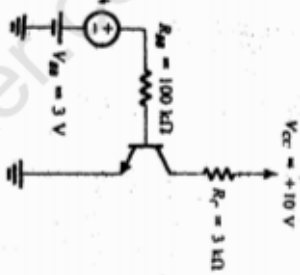


Fig.(4)

- (c) Explain the effect of each capacitor of a CE amplifier with the gain frequency curve. Also discuss the low frequency response of a CE amplifier.

1314061

5

IC