



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131403-N

Roll No.

B. Tech.

(SEM. IV) THEORY EXAMINATION, 2014-15
ELECTRONIC MEASUREMENTS AND INSTRUMENTATION

Time : 3 Hours] [Total Marks : 100

- Note : (1) Attempt all questions.
(2) All questions carry equal marks.

- 1 Attempt any four parts : 5×4=20
(a) Define measurement. Calculate percentage error in determination of time period of a pendulum given by

$$T=2\pi\sqrt{\frac{l}{g}}$$

Where l and g are measured in ± 2% and ± 3% errors.

- (b) Differentiate between Gross errors and Systematic errors. List a few ways of minimizing the effect of errors in measurement.
(c) A batch of resistors that each have a nominal resistance of 330Ω are to be tested and classified as ± 10 % components at 25 °C. If their temperature coefficient is -300ppm/ °C, calculate the maximum and minimum resistance for these components at 100 °C.

- (d) A thin wire has a length of 21.7 cm and radius 0.46 cm. Calculate the volume of the wire correct to required significant figures. 10×2=20
- (e) Explain the construction of a PMMC instrument. Mathematically prove that the scale of such an instrument is linear.
- (f) Explain the concept of Swamping resistance. What are the materials generally used for manufacturing these resistances.
- 2 Attempt any four parts : 5×4=20
- (a) What do you mean by Loading Effect? How does electronic voltmeter help in minimizing the loading effect?
- (b) Draw and explain the FET input voltmeter circuit with range changing.
- (c) Explain the -working of precision rectifier based voltmeters.
- (d) A Half wave rectifier Op-Amp based voltage amplifier circuit has a feedback resistance of 2.4kΩ and a
- 3 Attempt any two parts : 10×2=20
- (a) Give numerical example to explain the sensitivity of a Wheatstone bridge. What is the main advantage of using Kelvin's bridge over Wheatstone bridge?
- (b) Explain how AC bridges are balanced with proper phase diagrams. Derive the expressions of converting series inductor circuits into parallel equivalent circuits.
- (c) Write the mathematical expressions for inductor Q-factor and capacitor D-factor. Explain the working of inductance Comparison Bridge.
- 4 Attempt any two parts: 10×2=20
- (a) Draw and explain the block diagram of Oscilloscope automatic time base with proper waveforms at the output of each block.
- (b) Explain the operation of Sampling Oscilloscopes. Also explain individual circuits of staircase generator and sampling gate.
- (c) What do you mean by interpolation? Briefly explain the operation of a DSO storage and display system.
- 5 Attempt any two parts: 10×2=20