



Printed Pages: 6

om

EEC-401/EC-401 (MTU)

om

(Following Paper ID and Roll No. to be filled in your Answer Books)

Paper ID : 131401

Roll No.

--	--	--	--	--	--	--	--	--	--

B.TECH.

Theory Examination (Semester-IV) 2015-16

ELECTRONICS CIRCUITS

Time : 3 Hours

Max. Marks : 100

Note : Attempt all Sections.

Section-A

1. This question consist of short answer questions. Attempt all parts. All parts carry equal marks. (2×10 = 20)

- (a) What is Op-amp? Give its equivalent circuit.
- (b) For NMOS transistor, write the drain current expression for all its region.
- (c) Draw a high frequency T model of n-channel MOSFET incorporating output resistance.

(1)

P.T.O.





- (d) Draw the circuit diagram for CB amplifier.
- (e) Calculate  $\beta$  and  $\alpha$  for a transistor if emitter current is 10mA and collector current is 9mA.
- (f) Define input offset voltage of MOS differential pair.
- (g) Explain why voltage divider biasing is preferred.
- (h) Define Unity gain frequency.
- (i) Draw a large-signal equivalent circuit model NPN transistor, incorporating the output resistance.
- (j) Give the Barkhausen conditions to obtain sustained oscillations.

## Section-B

2. Attempt any FIVE questions. All questions carry equal marks. [10×5=50]

- (a) (i) Define and give the significance of Slew rate and CMRR. For an op-amp having a slew rate of 60 V/ $\mu$ s, what is the highest frequency at which a 20V



peak to peak sine wave can be produced at the output?

- (ii) Describe the characteristics of an Op-amp. Draw the circuit diagram of difference amplifier using op-amp and calculate the differential gain ( $A_d$ ), common mode gain ( $A_{cm}$ ) and differential input resistance ( $R_{id}$ ).
- (b) (i) Describe classification of output stage power amplifier. Describe the methods of biasing for class AB power amplifier.
- (ii) What do you mean by cross over distortion. Describe how can it be overcome.
- (c) Describe the construction and operation of N-channel enhancement MOSFET. Describe the role of substrate (the body effect) in MOSFET.
- (d) Draw the high frequency equivalent circuit model for the MOSFET and list all MOSFET internal Capacitances.
- (e) (i) Give the circuit for CC amplifier and calculate  $R_{in}$  and  $R_{out}$  for the CC amplifier.



- (ii) Draw the circuit diagram of CB amplifier and calculate expression for short-circuit current gain with T-model.
- (f) (i) Discuss the various internal capacitances for BJT. A particular small geometry BJT has  $f_T$  of 5 GHz and  $C_\mu = 1$  pF when operated at  $I_C = 0.5$  mA. What is  $C_\pi$  in this situation? Also find  $g_m$ . For  $\beta = 150$ , find  $r_\pi$  and  $f_\beta$ .
- (ii) Draw the circuit diagram of a Wien-bridge oscillator and derive an expression for the frequency of oscillations.
- (g) (i) Explain the operation of MOS differential pair with differential input voltage. Also calculate the range of input differential signals.
- (ii) For the active loaded BJT differential amplifier let  $I = 0.8$  mA,  $V_A = 100$  V and  $\beta = 160$ . Find  $G_m$ ,  $R_o$ ,  $A_d$  and  $R_{id}$ .
- (h) (i) Design a series – shunt feedback amplifier and derive expressions for  $A_T$ ,  $R_{of}$  and  $R_{ir}$ .
- (ii) For the Colpitt's oscillator, derive an expression for the frequency of oscillation.



Attempt any TWO questions. Each question carry equal marks.

(15×2=30)

3. (a) Explain the effect of finite open loop gain and bandwidth on the circuit performance. Calculate the frequency response of closed loop inverting amplifier.
- (b) Explain the working of BJT as an amplifier and as a switch with the help of neat diagram and necessary equations. Also calculate the amplifier gain.
4. (a) Discuss a common- source amplifier, draw its ac equivalent circuit and obtain expression for its terminal characteristics.
- (b) Describe the operation of class B push-pull power amplifier giving its circuit, also obtain its efficiency.
5. (a) Draw the NMOS differential amplifier with a common-mode input signal and calculate the common Mode Gain and CMRR. Also explain the effect of  $R_D$  mismatch on CMRR.



- (b) Explain the merits and demerits of negative feedback. Also explain in brief the various topologies used in negative feedback.

firstRanker.com