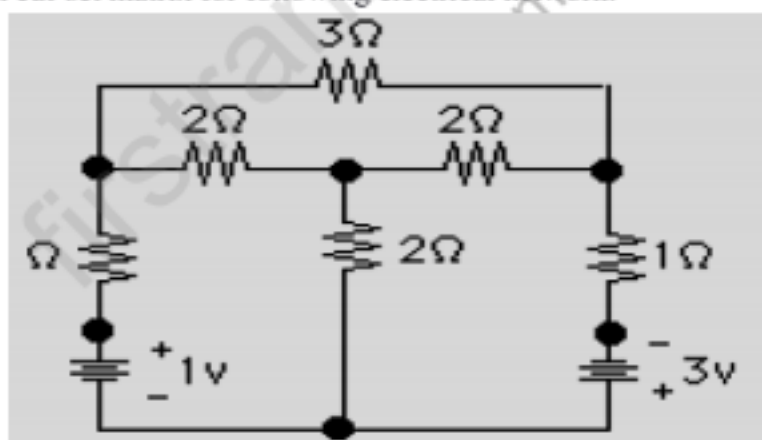


B. TECH.
**THEORY EXAMINATION (SEM-IV) 2016-17
NETWORK ANALYSIS AND SYNTHESIS**
Time : 3 Hours
Max. Marks : 100
Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.
SECTION – A
1. Attempt all of the following questions:
10 x 2 = 20


- (a) Define a two port network.
- (b) Define network synthesis.
- (c) What do you mean by transfer function?
- (d) Define twig and link.
- (e) Write a definition of convolution.
- (f) How you can say that a network is stable .Give definition.
- (g) What do you mean by filters?
- (h) Give statement of superposition theorem.
- (i) Write down all the properties of loop impedance matrix.
- (j) Define tree in graph theory.

SECTION – B
2. Attempt any five of the following questions:
5 x 10 = 50


- (a) Explain Z-impedance parameter in detail.
- (b) Give classification of filters.
- (c) Obtain cut-set matrix for following electrical network.



- (d) Determine the z-parameters of fig.

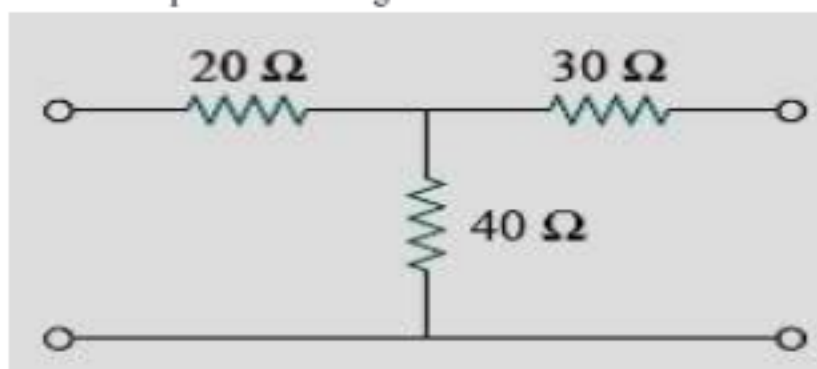

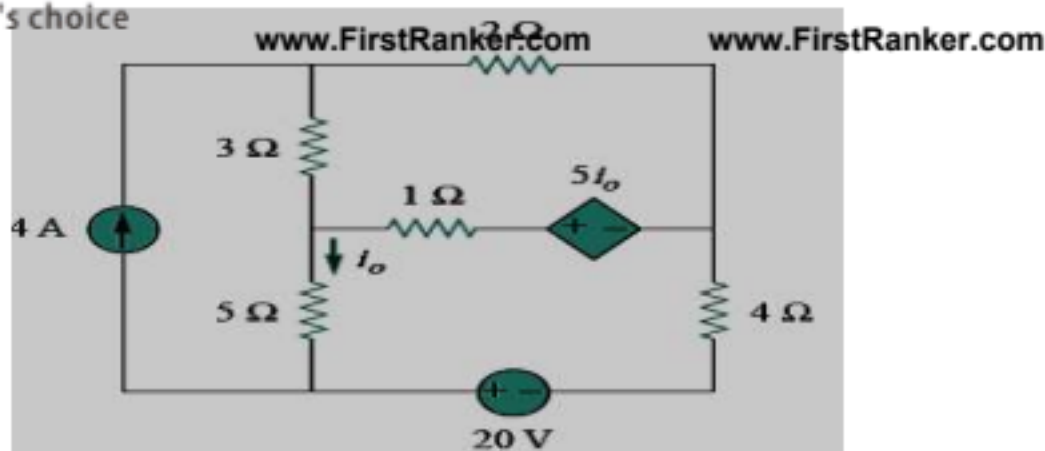- (e) Find i_o in the circuit in Fig. using superposition theorem.




- (f) Explain admittance parameters in detail
- (g) Explain in detail band stop filter, with prove.
- (h) Give statement and prove maximum power transfer theorem.

SECTION – C

Attempt any two of the following questions:

2 x 15 = 30

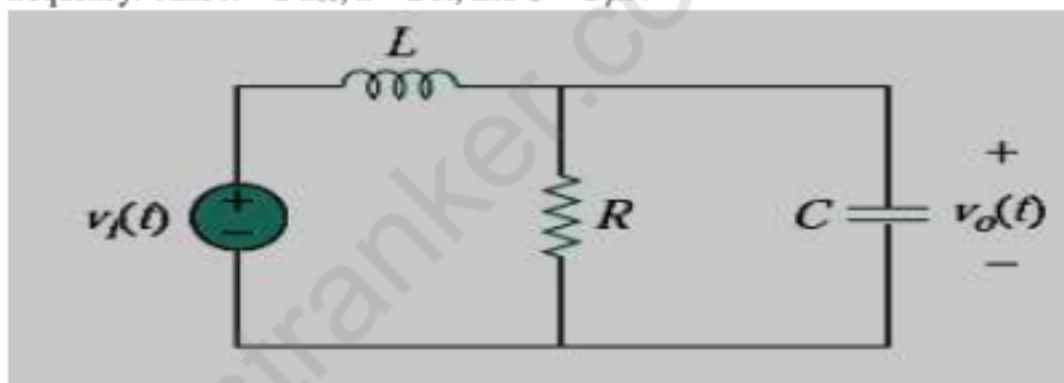- 3 With example explain first Foster form realization of LC networks.
- 4 Determine what type of filter is shown in Fig. 14.39. Calculate the corner or cutoff frequency. Take $R = 2\text{ k}\Omega$, $L = 2\text{ H}$, and $C = 2\text{ }\mu\text{F}$.



- 5 Obtain Cauer form realization of following and obtain network.

$$Z(s) = \frac{(s+1)}{s(s+2)}$$

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$