

Printed Pages : 4

387

NEC-501

(Following Paper ID and Roll No. to be filled in your Answer Book)

Paper ID :131501

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech

(SEM. V) (ODD SEM)

THEORY EXAMINATION, 2015-16

INTEGRATED CIRCUITS

Time:3 hours]

[Maximum Marks:100

Section-A

1. Attempt all parts. All parts carry equal marks. Write answer of each part in short. (2x10=20)
- (a) Why don't we normally realize the beta-compensated current mirror using MOS?
 - (b) What are the basic blocks of phase-locked loop?
 - (c) What do you understand by hysteresis voltage?
 - (d) What is the role of coupling capacitor (C_c) in IC 741 internal circuit?
 - (e) Give the example of a square wave generator which utilizes positive feedback.
 - (f) What is capture range in PLL?

(1)

NEC-501 / 11600

- (g) What is the chip number for phase locked loop?
- (h) Define the term V_m and V_n for the CMOS inverter.
- (i) The basic step of 9 bit DAC is 10.3mV. if 000000000 represents 0 V, what output is produced if the input is 101101111?
- (j) Define noise margin for the CMOS inverter.

Section-B

Note: Attempt any five questions from this section.

(10x5=50)

- What do you understand by the base current compensated current mirror? How does it provide improvement over simple current mirror circuit? Explain with the help of a neat circuit diagram.
- Define the slew rate. Also derive the relationship between f_t and slew rate for the IC 741.
- Sketch the properly labeled Master Slave D flip-flop circuit and explain its operation with the help of proper waveform of the clock signal.
- What is a DAC? Describe the weighted resistor DAC. Give mathematical expressions in support of your answer.

(2)

NEC-501

6. Determine I_{C1} , I_{C2} , I_{C3} for the circuit shown in figure 1. Assume $\beta = 125$.

 


Figure 1

- Draw the functional block diagram of IC 555 and explain its working. Design a 555 timer as an Astable multivibrator with an output signal timer frequency of 700 Hz and 60% duty cycle.
- Describe the Antoniou inductance simulation circuit with properly labelled circuit diagram and give mathematical expressions in support of your answer.
- Describe the sample and hold circuit with the help of an op-amp. What are the applications of sample and hold circuit?

(3)

P.T.O.

Section-C

Note: Attempt any two questions from this section.

(15x2=30)

10. Describe the circuit for the KHN filter using three op-amp. Design a second order butterworth low-pass filter having upper cut-off frequency 1kHz. Determine its frequency response.

11. Describe different regions of operation for CMOS inverter over its VTC characteristics.

Consider a CMOS inverter with following parametrs :

$$V_{DD} = 3.3 \text{ V}, V_{T0,n} = 0.6 \text{ V}, V_{T0,p} = 0.7 \text{ V}, K_n = 200 \mu \text{ A/V}^2, K_p = 80 \mu \text{ A/V}^2$$

Calculate the noise margin of the CMOS inverter circuit.

12. Describe the Schmitt trigger with the help of proper circuit diagram and transfer characteristics. A Schmitt trigger with the upper threshold level $V_{UT} = 0 \text{ V}$ and hysteresis width is 0.2V converts 1kHz sine wave of amplitude $4V_{pp}$ into a square wave. Calculate the time duration of the negative and positive portion of the output waveform.

—X—

(4)

NEC-501 / 11600