

Printed Pages : 3



EEC604

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131604

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. VI) THEORY EXAMINATION, 2014-15

INTRODUCTION TO ELECTRIC DRIVES

Time : 2 Hours]

[Total Marks : 50

1 Attempt any two parts : 2×5=10

(a) Explain the various terms involved in turn on and turn off time of SCRs in dynamic characteristics. Why circuit turn off time is kept larger ?

(b) Define di/dt and dv/dt protection of SCRs. What are the components used to protect SCR ?

(c) Give various triggering methods in SCR. Explain in detail pulse triggering method and requisite method.

2 Attempt any two parts of the following : 2×5=10

(a) Derive the expression of a 1-phase full wave bridge rectifier fully controlled for RLE load and also draw the requisite waveforms.

131604]

1

[Contd...

- (b) Explain the operation of three phase half controlled full wave rectifier with desired waveforms.
- (c) Explain control strategies of chopper with respect to step down chopper. Also classify and explain the choppers according to quadrant operation.

3 Attempt any two parts of the following : 2×5=10

- (a) Give the difference between 180° and 120° modes of three phase inverter with relevant waveforms of phase and line voltages.
- (b) Explain the basic principle of step down cycloconverter.
- (c) Write short notes on following :
 - (i) Series inverter
 - (ii) Jones chopper
 - (iii) $3-\phi$ to $3-\phi$ step down cycloconverter.
 - (iv) Power factor improvement in dc drives.
 - (v) Self control scheme of synchronous motor drive.

4 Attempt any two parts of the following : 2×5=10

- (a) The speed of separately-excited dc motor is controlled through 1-phase half wave controlled from 230 V mains. The motor armature resistance is 0.5 Ohm and motor constant is $K = 0.4 \text{ V-s/rad}$ for load torque of 20 Nm at 1500 rpm and for constant armature current, calculate :
 - (i) Firing angle of converter.
 - (ii) RMS value of thyristor current.
 - (iii) I/P power factor of the motor.

1316041

2

[Contd...

- (b) Describe the regenerative braking of chopper fed separately excited dc motor. Illustrate the answer with circuit diagram and relevant waveforms.
- (c) Define the basic principle of operation of cyclo-converter. Explain the working of 1-phase and 3-phase cycloconverter.

5 Attempt any two parts of the following : 2×5=10

- (a) Explain four quadrant chopper drives. Explain three phase semiconductor drives.
- (b) Enumerate the various methods of speed control of 3-phase induction motor when fed through semiconductor devices.
- (c) Describe the Kramer drive and show that steady state torque is not influenced by whether a transformer is used or not ?

1316041

3

[3450]