

[Contd...

1

121603]

- (f) Explain working of Triac.  
(e) Explain the steady state and switching characteristics of MOSFET.  
(d) Explain the significance of latching and holding currents.  
(c) derating factor of 14% and current rating of 7.5KV and 1 KA. Assume parallel combination for a circuit for a total voltage 500V and 75A required for each branch of a series of thyristors each with a rating of 500V and 75A.  
(b) Explain the switching characteristics of a BJT.  
(a) What are the characteristics of an ideal power switching device?
- Attempt any four parts: 5×4=20

Note: (1) Attempt all questions.  
(2) All questions carry equal marks.

[Total Marks : 100

Time : 3 Hours]

**POWER ELECTRONICS**  
(SEM. VI) THEORY EXAMINATION, 2014-15  
**B. Tech.**

Roll No.									
PAPER ID : 121603									
(Following Paper ID and Roll No. to be filled in your Answer Book)									

EEE-602



Printed Pages : 3

2. Attempt any two parts :

10×2=20

- (a) What is a DC chopper? Describe the various types of chopper configuration with neat and appropriate diagrams.
- (b) Discuss the two transistor model of a thyristor. Using this model, describe the various mechanisms of turning on a thyristor.
- (c) Explain the resonant pulse commutation with the help of circuit diagram and waveforms. Explain the effect of accelerating diode.

3. Attempt any two parts:-

10×2=20

- (a) A single phase half controlled bridge operated from the 230 V, 50 Hz mains feeds a resistive load of 100  $\Omega$ . If the firing angle is 60°, Calculate,
  - (i) Average output voltage
  - (ii) rms output voltage
  - (iii) total output power
  - (iv) DC output power
  - (v) load current at instant of turn on
- (b) What do you understand by dual converters? Explain the operation of a 3  $\phi$  dual converter using circulating current mode of operation. How are firing angles of two converters controlled?
- (c) Discuss the working of 1  $\phi$  full wave ac-dc converter taking into account the effect of source inductance. Draw the output voltage waveform for firing angle of 30°.

121603]

2

[Contd...

4. Attempt any two parts:-

10×2=20

- (a) Describe the basic principle of working of 1  $\phi$  to 1  $\phi$  step down cycloconverter for both continuous and discontinuous conduction. Make the conduction of various thyristor also.
- (b) Describe 1  $\phi$  ac voltage controller with inductive and resistive loads. Describe an expression for output voltage.
- (c) Show that the fundamental rms value of per phase output voltage of low frequency for an m pulse cycloconverter is given by:  

$$V_{oV} = V_{phm} \pi \sin \frac{\pi}{m}$$

5. Attempt any two parts:-

10×2=20

- (a) Discuss the working principle of a 1  $\phi$  series inverter. What are the advantages and disadvantages of series inverter.
- (b) Explain operation of a 3  $\phi$  bridge inverter employing 1200 mode of operation. Draw waveforms of phase voltages and any one line voltage assuming star connected resistance load.
- (c) The single phase quasi-square wave bridge inverter operates from a DC supply of 200V at a frequency of 100 Hz and feeds a resistive load of 10  $\Omega$  calculate:
  - (i) Duration of the ON period if the rms value of the load voltage is 100V.
  - (ii) Peak supply current
  - (iii) Average DC supply current

121603]

3

[ 8675 ]