



B.TECH.

THEORY EXAMINATION (SEM-VI) 2016-17

ANALOG SIGNAL PROCESSING

Time : 3 Hours

Max. Marks : 100

Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.

SECTION A

1 Attempt all parts:

(10X2=20)

- What do you understand by impedance?
- Differentiate between digital and analog signal.
- Explain filter with example.
- What is biquads? Explain.
- Explain signal rectification.
- What do you mean by peak and valley?
- Define transconductance.
- What is grounded inductor?
- Define voltage limiter circuit.
- Define gyrator with example.

SECTION B

2 Attempt any FIVE parts:

(10X5=50)

- Discuss the differentiation and addition linear analog function with an example.
- Write a note on the impedance transformation and conversion with an example.
- Illustrate the process of signal rectification with using an appropriate example.
- What do you mean by a logarithmic amplifier? Discuss.
- Explain Notch and AP transfer functions with an example.
- Describe the working of op-amp as an amplitude demodulator.
- Write a note on the amplitude demodulation.
- What do you mean by ladder design? Illustrate with an example.

SECTION C

Attempt any TWO questions:

(15X2=30)

- What do you understand by generalized convertor? Discuss it in detail using suitable example with the block diagram.
- What are the methods for detecting peaks and valleys? Describe any methods for detecting peaks and valleys with an example.
- Write detailed note on the following:
 - C-filters.
 - Voltage limiting.