



B.TECH.

THEORY EXAMINATION (SEM-VIII) 2016-17

DIGITAL SYSTEMS USING VHDL

Time : 3 Hours

Max. Marks : 100

Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.

SECTION – A

1. Explain the following:

10 x 2 = 20

- (a) Differentiate between Combinational and Sequential Circuits.
- (b) Write Application and Advantages of VHDL
- (c) Write VHDL code for Full Adder using structural style of modelling.
- (d) What are Generic parameters?
- (e) Write VHDL code for 4:2 encoder using Behavioural style of modelling.
- (f) What are different levels of abstractions of digital design?
- (g) Define Lexical elements, signals and Variable.
- (h) What is inertial delay?
- (i) Write the VHDL code for 2:4 MUX in structural style
- (j) What are binding alternatives?

SECTION – B

2. Attempt any five parts of the following questions:

5 x 10 = 50

- (a) Explain Delta delay and transaction appending rules.
- (b) Discuss Sequential modelling and attributes.
- (c) What is basic structure of VHDL? Write the VHDL code for 4:16 multiplexer.
- (d) Write VHDL code for 16 bit SIPO Shift register.
- (e) What are synthesis rules and styles for hardware core and models?
- (f) Write VHDL code for D Flip Flop.
- (g) What is Guarded signal Assignment? Explain with example.
- (h) Explain inertial and transport delay mechanism with comparison.

SECTION – C

Attempt any two parts of the following questions:

2 x 15 = 30

- 3 Explain Testing and its different issues related to design test
- 4 Write the behavioural VHDL code for RAM.
- 5 Explain logic behind floating point multiplication.

