



M.Tech I Semester Regular & Supplementary Examinations January/February 2019

STRUCTURAL DIGITAL SYSTEM DESIGN

(Common to DECS, ECE, DSCE, ES, VLSI&ES, ES&VLSI, VLSI&ESD, VLSI, VLSIS and VLSISD)

(For students admitted in 2017 & 2018 only)

Time: 3 hours

Max. Marks: 60

Answer all the questions

- 1 (a) Implement the following Boolean function using 8:1 multiplexer.

$$F(A, B, C, D) = \sum m(1, 2, 4, 6, 7, 11, 13, 15)$$

- (b) What is the need of ALU and explain about it?

OR

- 2 Construct a 5 to 32 line decoder with four 3 to 8 line decoders with enable and a 2 to 4 line decoder.

- 3 (a) Explain top-down design methodology with example.

- (b) Discuss about the separation of controller and architecture.

OR

- 4 What are the basic elements of ASM chart explain clearly with an example?

- 5 Briefly explain about multiplexer controller method and one shot method.

OR

- 6 Briefly discuss about fault diagnosis and testing with flow diagram.

- 7 Discuss about the 2910 micro program sequencer.

OR

- 8 Explain about design of micro programmed minicomputer.

- 9 Write short notes on simulators and schematic entry.

OR

- 10 Design a system for serial to parallel data conversion.
