



M.Tech I Semester Supplementary Examinations August/September 2018

**DIGITAL SYSTEM DESIGN**

(Common to DSCE, DECS, ECE, VLSIES, ESVLSI, VLSIESD & MNE)

(For students admitted in 2013, 2014, 2015 & 2016 only)

Time: 3 hours

Max. Marks: 60

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 Develop an ASM chart to design control logic of a binary divider and realize the same.
- 2 (a) Design an iterative comparator circuit to compare two  $n$  bit numbers.  
(b) How a sequential circuit can be designed using FPGA?
- 3 Explain about the following types of faults:  
(a) Stuck at faults.  
(b) Bridge faults.  
(c) Temporary faults.
- 4 (a) Discuss in detail Boolean difference method in combinational circuits.  
(b) What is the significance of Kohavi algorithm? Explain how it detects multiple faults in two-level-networks with a simple example.
- 5 Classify the fault detection experiments for the sequential circuits and explain.
- 6 Design a 3-bit BCD to grey code converter and realize the circuit using PLA and then show that how folding will reduce the number of cross points given on the PLA.
- 7 Explain in detail testable PLA design with an example.
- 8 The output  $Z$  of a fundamental-mode, two input sequential circuit is to change from 0 to 1 only when  $X_2$  changes from 0 to 1 while  $X_1 = 1$ . The output is to change from 1 to 0 only when  $X_1$  changes from 1 to 0 while  $X_2 = 1$ . (i) Find a minimum-row reduced flow table, the output should be fast and flicker-free. (ii) Show a valid assignment and write a set of (static) hazard-free excitation and output equations.

\*\*\*\*\*