

Code: 9D06203

M.Tech II Semester Supplementary Examinations February 2018

DESIGN OF FAULT TOLERANT SYSTEMS

(Digital Systems and Computer Electronics)

(For students admitted in 2012, 2013, 2014, 2015 & 2016 only)

Time: 3 hours

Max. Marks: 60

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Derive relation between reliability and MTBF.
(b) Derive reliability of the following systems:
(i) Series. (ii) Parallel. (iii) Parallel-series. (iv) Series-parallel.
- 2 (a) Discuss about static and dynamic redundancy techniques with neat diagrams.
(b) Discuss about self purging redundancy technique.
- 3 (a) Design a totally self checking checker.
(b) Design a self checker circuit using m out of n codes.
- 4 Give the design procedure for a totally self checking PLA.
- 5 (a) Define the terms: (i) Testability. (ii) Observability.
(b) Discuss about Reed Muller's expansion technique with an example.
- 6 With a neat diagram, discuss about a signature analyzer using an LFSR.
- 7 With a neat diagram, discuss about level sensitive scan design (LSSD).
- 8 Write short notes on the following:
(a) Exhaustive testing.
(b) Pseudorandom testing.
