

Code: 9D06206c

M.Tech II Semester Supplementary Examinations February 2018

FPGA ARCHITECTURE & APPLICATIONS

(Digital Systems and Computer Electronics)

(For students admitted in 2012, 2013, 2014, 2015 & 2016 only)

Time: 3 hours

Max. Marks: 60

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Implement the following Boolean function using PAL:

$$F(w, x, y, z) = \sum_m (0, 2, 4, 6, 8, 10, 11, 12, 14, 15)$$

- (b) Distinguish between FPGA and CPLD.

- 2 (a) Explain a Govt. state assignments for FPGA.

- (b) Realize switching functions (2, 3, 4, 6, 7) using 2 input LUTs. Give the truth table implementation in each LUT & show wires in FPGA.

- 3 (a) Write about FPGA and compare speed performance of ACT1, ACT2, ACT3 FPGA.

- (b) What is LE? Draw and explain the working of LE of altera FLEX 8000.

- 4 (a) What is state transition table?

- (b) Explain how state transaction assignment can be carried at for FPGA.

- 5 (a) Explain the procedure for design of a state machine using one-hot encoding.

- (b) Explain the symbolic representation of FSM architectures.

- 6 Write notes on:

- (a) Architecture centred around non registered PLDs.

- (b) State machine design centered around shift registers.

- 7 (a) Design a parallel adder sequential circuit.

- (b) Explain multiplexers.

- 8 Write notes on:

- (a) Counters and parallel controllers.

- (b) Combinational logic circuits.
