

Code: 13A02101

B.Tech I Year (R13) Supplementary Examinations June 2016

ELECTRICAL CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 hours


Max. Marks: 70

PART – A


(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

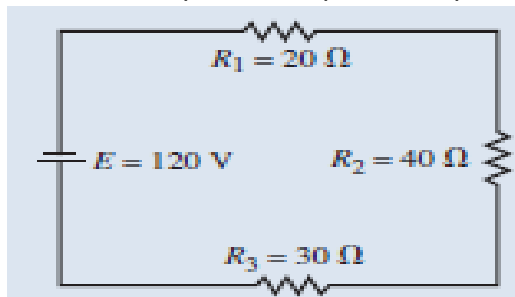
- (a) Show that the power dissipated is equal to the power delivered.



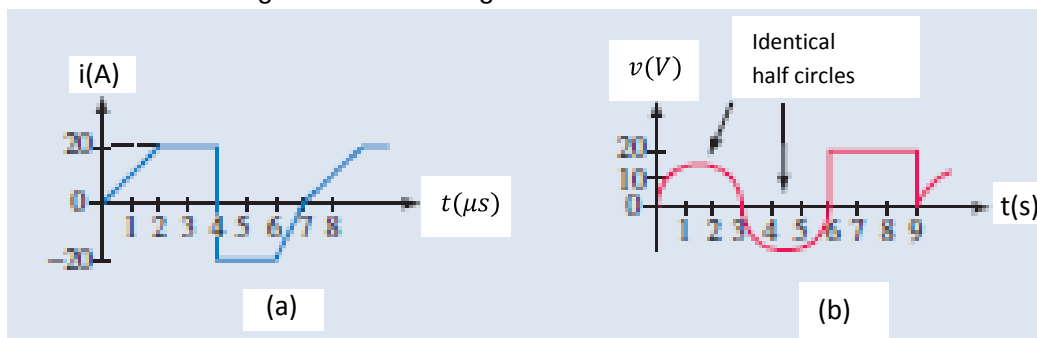- (b) Define Self inductance.
 (c) A voltage source has internal impedance $(4+j5)$ ohm. Find the load impedance for maximum power transfer.
 (d) Determine the averages for the circuit given below:



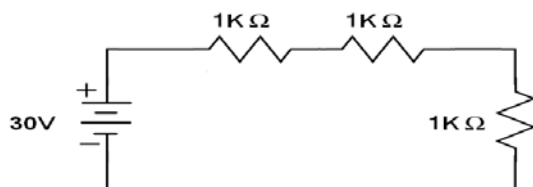- (e) A resistance 5 ohms, inductance 0.02 H and capacitor $5\mu\text{F}$ are connected in series. Find the resonance frequency and the power factor at resonance.
 (f) Three identical resistors of $20\ \Omega$ each are connected in star to a 415 V, 50 Hz, three-phase supply, calculate the total power consumed, If they are connected in delta.
 (g) Obtain the dual circuit for the below figure.



- (h) State Thevenin's theorem.
 (i) Define time constant for RL & RC circuits.
 (j) A series RLC circuit with $R = 10\ \Omega$, $L = 2\ \text{H}$ and $C = 1\ \text{F}$ has a constant voltage of 100 V applied at $t = 0$. Determine the initial values of $i(t)$ and $di(t)/dt$.

Contd. in page 2

PART - B


(Answer all five units, 5 X 10 = 50 Marks)

UNIT - I


- 2 The number of turns in a coil is 250. When a current of 2 A flows in this coil, the flux in the coil is 0.3 mWb. When this current is reduced to zero in 2 ms, the voltage induced in a coil lying in the vicinity of coil is 63.75 volts. If the coefficient of coupling between the coils is 0.75, find self-inductance of the two coils, mutual inductance and number of turns in the second coil.

OR

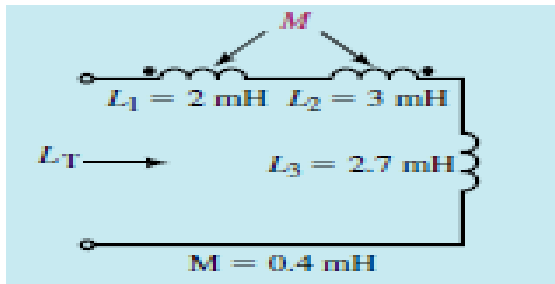- 3 (a) Three inductors are connected in series (Figure). Coils 1 and 2 interact, but coil 3 does not.
(i) Determine the effective inductance of each coil.
(ii) Determine the total inductance of the series connection.



- (b) Find the equivalent resistance between A & B for the circuit shown in figure below.

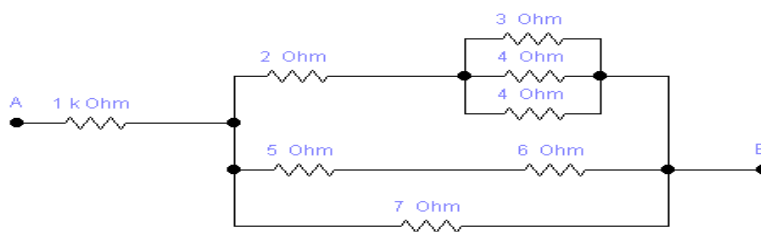**UNIT - II**


- 4 Derive the expression for RMS value and average value of an AC circuit.

OR


- 5 (a) Justify the line current is equal to $1/\sqrt{3}$ times of phase current under the balanced load condition
(b) Given $v = 20\sin(\omega t + 30^\circ)$ and $i = 18\sin(\omega t - 40^\circ)$, draw the phasor diagram, determine phase relationships and sketch the waveforms.

UNIT - III

- 6 For the series resonant circuit of figure given below:
(i) Find I , V_R , V_L , and V_C at resonance. (ii) What is the Q_s of the circuit? (iii) If the resonant frequency is 5000 Hz, find the bandwidth. (iv) What is the power dissipated in the circuit at the half-power frequencies?

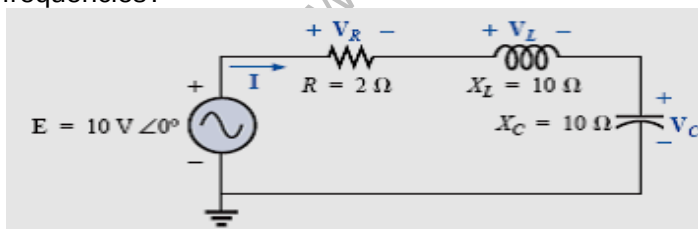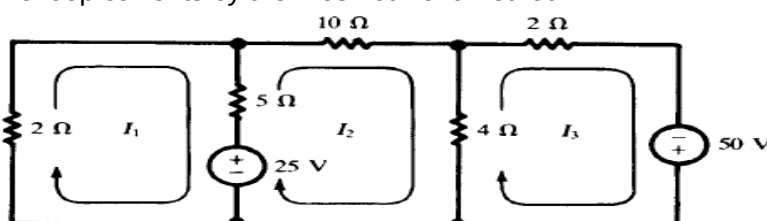
**OR**

- 7 Solve loop currents by the mesh current method.




UNIT - IV

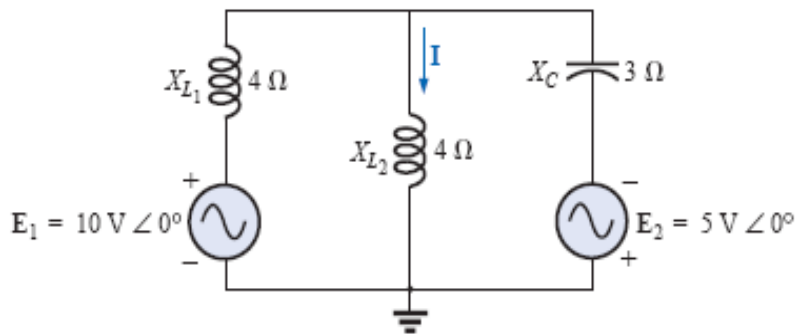- 8 Using the superposition theorem, find the current I through the 4Ω (X_{L2}).




OR

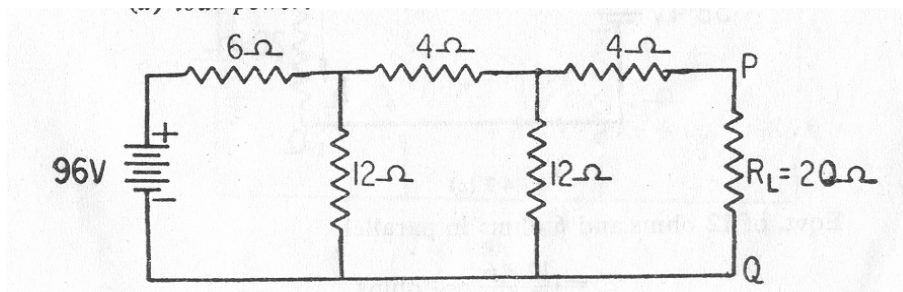- 9 For the following figure. Find the Thevenin equivalent circuit, load current and power consumed by load.



UNIT - V

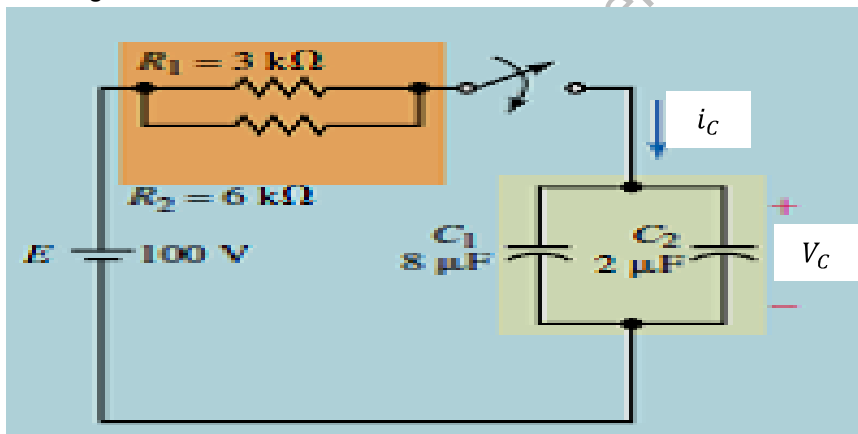- 10 For the circuit shown in figure below, determine expressions for V_C and i_C . Capacitors are initially uncharged.



OR

- 11 Derive the current response of series RL circuit.
